

---

# EE/CE 6301: Advanced Digital Logic

*Bill Swartz*

**Dept. of EE  
Univ. of Texas at Dallas**

---


# Session 11

## **Testing of Digital Systems**

---


# **VLSI Test Philosophy**

# Testing

 

# Test Philosophy

- A Pass/Fail test:

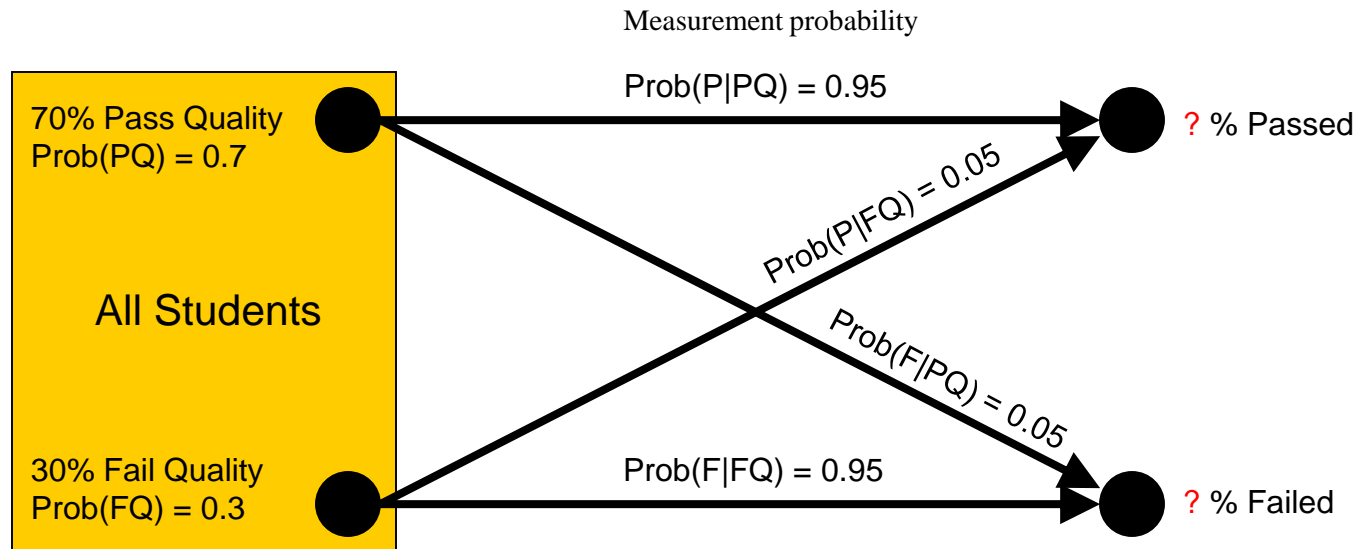

PQ: student is pass quality  
FQ: student is fail quality

P: student passes the test  
F: student fails the test

# Test Philosophy (cont'd)


---

- Probability of passing:

$$\begin{aligned}\text{Prob}(P) &= \text{Prob}(P | PQ) * \text{Prob}(PQ) + \text{Prob}(P | FQ) * \text{Prob}(FQ) \\ &= 0.95 * 0.70 + 0.05 * 0.30 = 0.68\end{aligned}$$

$$\begin{aligned}\text{Prob}(F) &= \text{Prob}(F | FQ) * \text{Prob}(FQ) + \text{Prob}(F | PQ) * \text{Prob}(PQ) \\ &= 1 - \text{Prob}(P) = 0.32\end{aligned}$$

- Student risk:

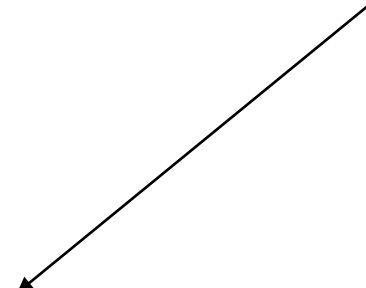
$$\Rightarrow \text{Prob}(PQ | F) = \frac{\text{Prob}(F | PQ) * \text{Prob}(PQ)}{\text{Prob}(F)} = \frac{0.05 * 0.7}{0.32} = 0.11$$

- 11% of failed students should have passed

$$\text{Prob}(A|B) = \frac{\text{Prob}(B|A) * \text{Prob}(A)}{\text{Prob}(B)} \quad \text{Bayes Theorem}$$

## Test Philosophy (cont'd)

---

- Student's risk (manufacturer's risk or **yield loss**):

$$\Rightarrow \text{Prob}(PQ | F) = \frac{\text{Prob}(F | PQ) * \text{Prob}(PQ)}{\text{Prob}(F)} = \frac{0.05 * 0.7}{0.32} = 0.11$$

- Teacher's risk (consumer's risk):

$$\Rightarrow \text{Prob}(FQ | P) = \frac{\text{Prob}(P | FQ) * \text{Prob}(FQ)}{\text{Prob}(P)} = \frac{0.05 * 0.3}{0.68} = 0.022$$


# VLSI Chips – Present and Future

Year	1997-2001	2003-2006	2009-2012
Feature Size, $\mu\text{m}$	0.25 – 0.15	0.13 – 0.10	0.07 – 0.05
Millions of Transistors/cm <sup>2</sup>	4 – 10	18 – 39	84 – 180
Number of wiring layers	6 – 7	7 – 8	8 – 9
Die Size, mm <sup>2</sup>	50 – 385	60 – 520	70 – 750
Pin count $\propto \sqrt{N_{\text{trans.}}}$	100 – 900	160 – 1475	260 – 2690
Clock Rate, MHz	200 – 730	530 – 1100	840 – 1830
Voltage, V	1.2 – 2.5	0.9 – 1.5	0.5 – 0.9
Power, W	1.2 – 61	2 – 96	2.8 – 109




 
# VLSI Fabrication Process

- A seed crystal is dipped into the melted silicon to initiate single-crystal growth
- Diameter: 75 – 230 mm
- Growth rate: 30 – 180 mm/hour
- The output is a silicon ingot
- Using diamond blades, the wafers are produced (thickness = 0.25 – 1 mm)
- At least one surface is polished to a flat, scratch-free mirror finish





# VLSI Fabrication Process (cont'd)

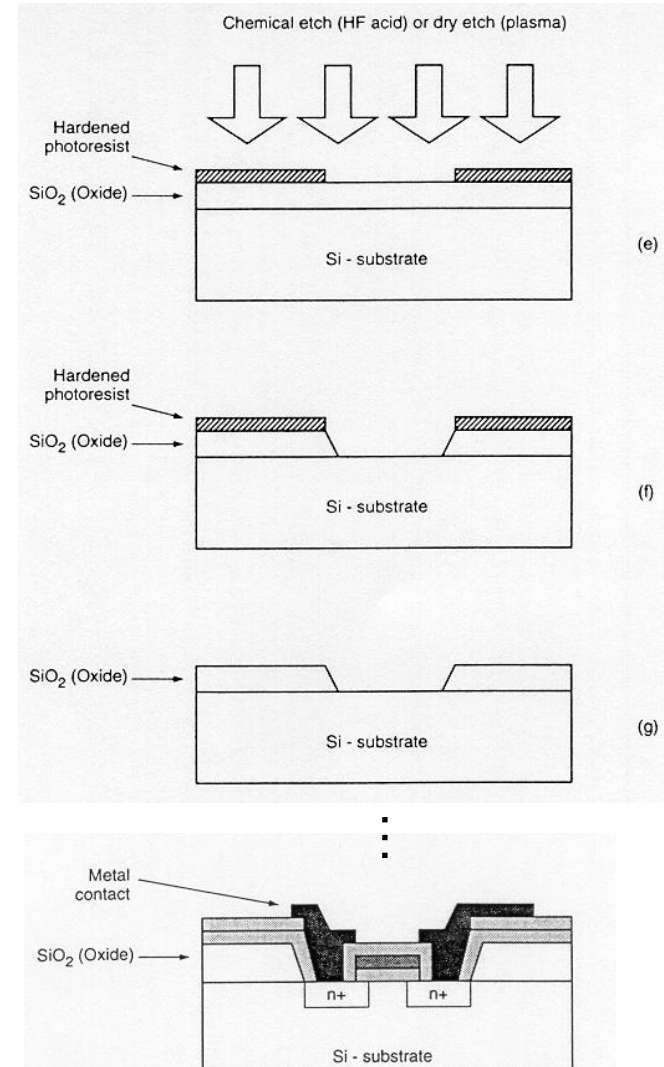 
  
# What May Go Wrong?

---

- Shorts between two points (bridges)
- Open in a line
- Improper doping
- Masking error
- Improper thickness of a line
- Particles on surface
- Electron migration due to heat
- Corrosion
- ...



# What Can be Done?

---

1. Wafer probe testing.
2. Use microscope to find faulty dices. Mark with a small ink. Reject after separation. Package the unmarked dies.
3. Test for electrical and mechanical characteristics.
4. Final inspection for cosmetic defects.
5. Pack and ship.



# Test Definition

---

- “Testing” of a system is an experiment in which the system is exercised and its resulting responses are analyzed to ascertain whether it behaved correctly
  - How to send input data (test patterns)?
  - How to collect output results (test signatures)?
  - How long the system should run?
  - How to make the conclusion?
  - How to locate the cause of misbehavior (diagnosis)?
  - What causes misbehavior?
  - What test equipment are needed?
  - ...

# Test Importance

---

- Test is an integral part of any manufacturing process.
  - Production Cost = Fabrication & Packaging + Testing
  - According to Semiconductor Industry Association (SIA) roadmap, the cost of testing a die will surpass its manufacturing cost in the near future.
- Each VLSI chip needs to be tested. Sampling is not adequate.

# When and Where to Test

---

- Try to detect defects at the earliest point possible.
- Costs increases dramatically (typically by an order of magnitude) as faulty components find their way to the higher level of integration
- Rule of 10:
  - \$1 to detect a faulty chip. Throw it out!
  - \$10 to find (and replace) a bad IC on a board.
  - \$100 to find a bad PC board in a system.
  - \$1000 to find a bad component in the fielded system

# Taxonomy of Testing

---

- Failure: incorrect operation of a system.
- Fault: the physical failure mechanism.
- Fault effect: the logical effect of a fault on a signal or carrying net.
- Error:
  - The condition (or state) of a system containing a fault, i.e. deviation from correct state (e.g. wrong component, incorrect wiring...).
  - An instance of an incorrect operation of a system



# **Taxonomy of Testing (cont'd)**

---

- An error does not necessarily lead to a failure.  
Example:
  - Error: existence of erroneous state of air pressure.
  - Failure: one of the operational tires on your car goes flat.
- Defect: physical problems due to imperfect manufacturing process.
  - Defects are not directly attributable to a human error.
  - Examples: shorts, opens, improper doping profiles, mask misalignment...
- Sometimes fabrication defects and errors are collectively referred to as physical faults

# **Taxonomy of Testing (cont'd)**

---

- Fault model: the basic assumptions regarding the nature of the logical (malignant) fault.
- A fault is “detected” by observing an error caused by it.
- Briefly:  
Defect → Fault → Error → Failure  
(e.g. dust particle → stuck-at-1 → erroneous logic value → circuit failing)

# **Taxonomy of Testing (cont'd)**

---

- Yield (Y): the probability (usually expressed as percent) that items (e.g. ICs) will not be defective (fraction of manufactured parts that is defect-free).
  - For VLSI chips yields range from 10% to 90% depending on the process, circuit complexity, lambda ( $\lambda$ ), etc.
  - $Y=1$  (100%) means defect free production.
  - $Y=0$  (0%) means all circuits are faulty.

# Taxonomy of Testing (cont'd)

---

- Fault coverage (FC) is a measure to grade the quality of a test:

$$\text{— FC} = \frac{\text{Number of faults detected}}{\text{Total number of faults}} * 100\%$$

— FC=1 (100%) : all possible faults detected

— FC=0 (0%) : no fault detected.

- Defect level (DL): the probability of shipping a defective product (the fraction of bad parts that pass all tests).

— An empirical equation:

$$DL = [1 - Y^{(1-FC)}] * 100\%$$

— Both Y and FC must be continually improved to maintain reliability of shipped products

---

# **Failure Rate (Fault Occurrence Frequency)**


# Type of Faults

---

- **Permanent fault:** always being present after their occurrence (in existence long enough to be observed at test time).
- **Intermittent fault:** existing only during some intervals (appears and disappears at regular intervals).
- **Transient fault:** a one-time occurrence, e.g. caused by a temporary change in some environmental factors (appears and disappears in short time intervals). These faults are crucial for real-time systems.

 
# Failure Rate Over Product Lifetime

- A well-known graphical representation of the failure rate, is the **bathtub curve**. It consists of three regions:
  1. Infant Mortality
  2. Working Life
  3. Wearout


 
# **Failure Rate Over Product Lifetime (cont'd)**

- **Infant mortality:** failures in this region are attributed to poor quality due to variations in the production process.
- **Working life:** Constant failure rate  $\lambda$ . Failures are considered to occur **randomly in time**.
- **Wear out:** Increasing failure rate. This represents the end-of-life period of a system.





# **Failure Rate Over Product Lifetime (cont'd)**

- It should be clear that a system should be shipped **after** it has passed the **infant mortality period**, in order to reduce the number of field returns.
- Shipping a system after the infant mortality period can be done by:
  1. Aging the system for that period (this can be several months)
  2. Aging the system under stress (this accelerates the aging process)


---

# **Test Economics**
 
# Repair Cost During the Product Phases


---

- A move from one product phase to the next causes the volume of parts and the test & repair cost to increase by a factor of *10*.  
*This is the rule-of-ten*


 
# Economics and Liability of Testing

- *Good tests*
  - reduce test & repair cost (see rule-of-ten)
  - can reduce development time & time-to market
  - can reduce field maintenance costs
  - reduce personal injury and law suits
- There is an optimum in test development cost and its contribution to profit. Too many tests require a long test development time and test cost



---

# **Main Fault Models**

# Goals of Fault Modeling

---

- To model physical defects in the circuit at high level of abstraction.
- To allow test generation and fault/coverage analysis to be done early in the design process.
- To model high percentage of the actual physical defects that can occur in components:
  - To reduce number of individual defects that have to be considered (e.g. find equivalent or dominant faults).
  - To reduce the complexity of the component/circuit description for test generation/analysis.


# Stuck-at Fault Model

---

- Most commonly used fault model.
- May consider “single” or “multiple” stuck-at faults.
- The components are assumed to be (internally) fault-free.
- The effect of faults is modeled by having a line segment tied to either:
  - Vcc (s-a-1)
  - GND (s-a-0)

# Stuck-at Fault Model (cont'd)

- Example:

 

- Fault-free function:  $f = x_1x_2 + x_2x_3$

- Faulty functions:

- Fault 1/0  $\rightarrow f^* = x_2x_3$

- Fault 2/1  $\rightarrow f^* = x_1 + x_3$

- Fault 6/0  $\rightarrow f^* = x_2x_3$

Line Segment  
Or  
Wire

Stuck-at Value



# Features of Single s-a-f Model

---

- Can be applied at the logic/RTL/system levels.
- Reasonable and manageable number of faults (i.e. less or equal  $2 * \#$  of line segments  $\approx 2 * \#$  of circuit nodes). So, is computationally feasible to deal with.
- Well-developed algorithms exist for automatic test pattern generation (ATPG)
- Other useful fault models like stuck-open, bridging, etc. can be applied into (sequence of) stuck-at faults

## Features of Single s-a-f Model (cont'd)

---


- Empirical evidence shows that single stuck-at fault model covers the majority (about 90%) of the possible manufacturing defects in circuits such as:
  - Source-drain shorts
  - Oxide pinholes
  - Diffusion contaminants
  - Metallization shorts
  - ...

# Other Fault Models

---

- Stuck-open fault
  - Assumption: a single physical line in the circuit is broken (usually internal to gates).
- Bridging fault
  - two (or more) lines are shorted together. The functional effect (on the logic nodes) is of a wired logic AND or OR depending on the technology
- Delay fault
  - Assumptions: The logic function of the circuit-under-test is error-free. Some physical defects (developed during fabrication) makes some delays in the circuit greater than some predefined bounds.


# Fault Analysis System

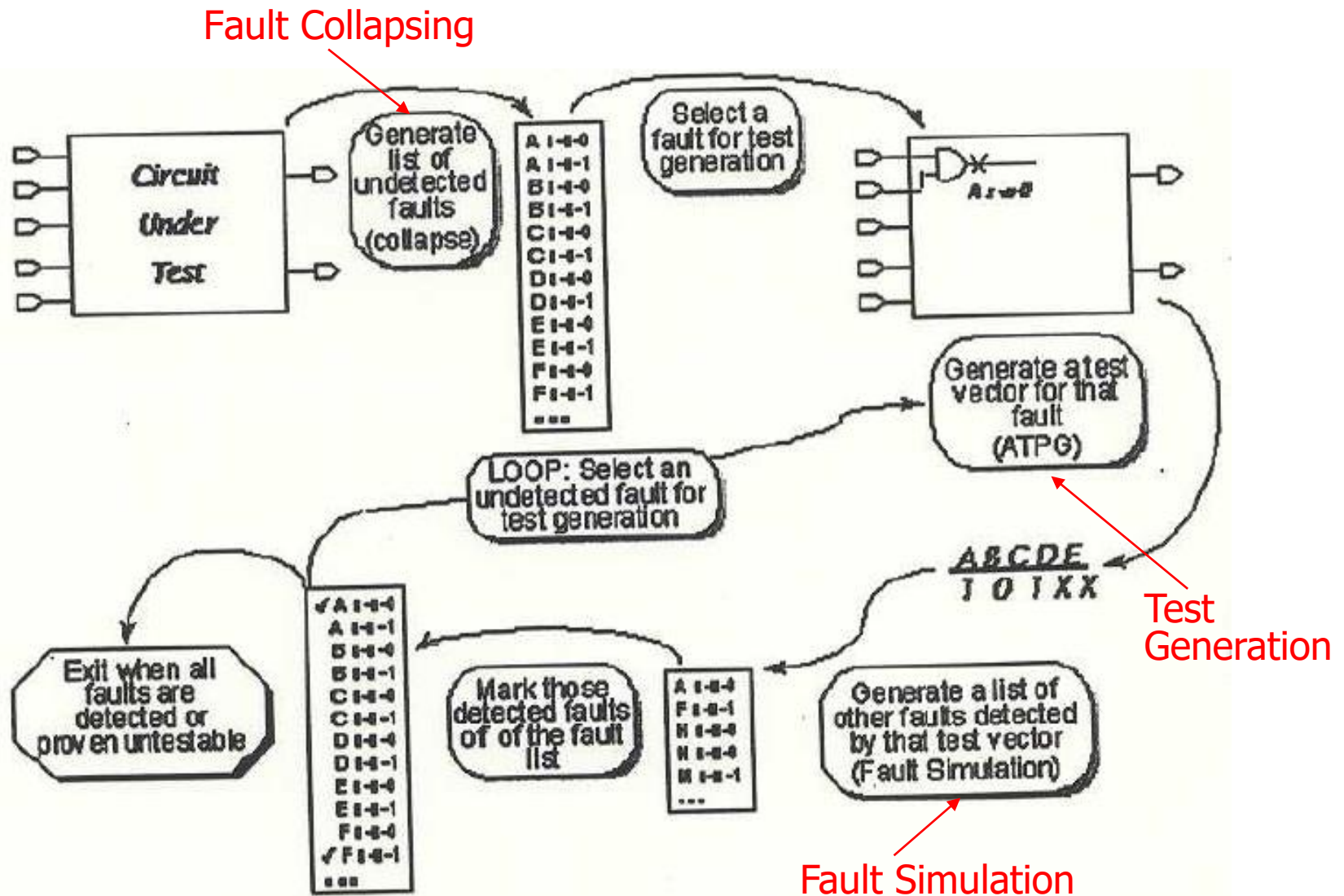

---

# **Fault Analysis System**

# Fault Analysis System

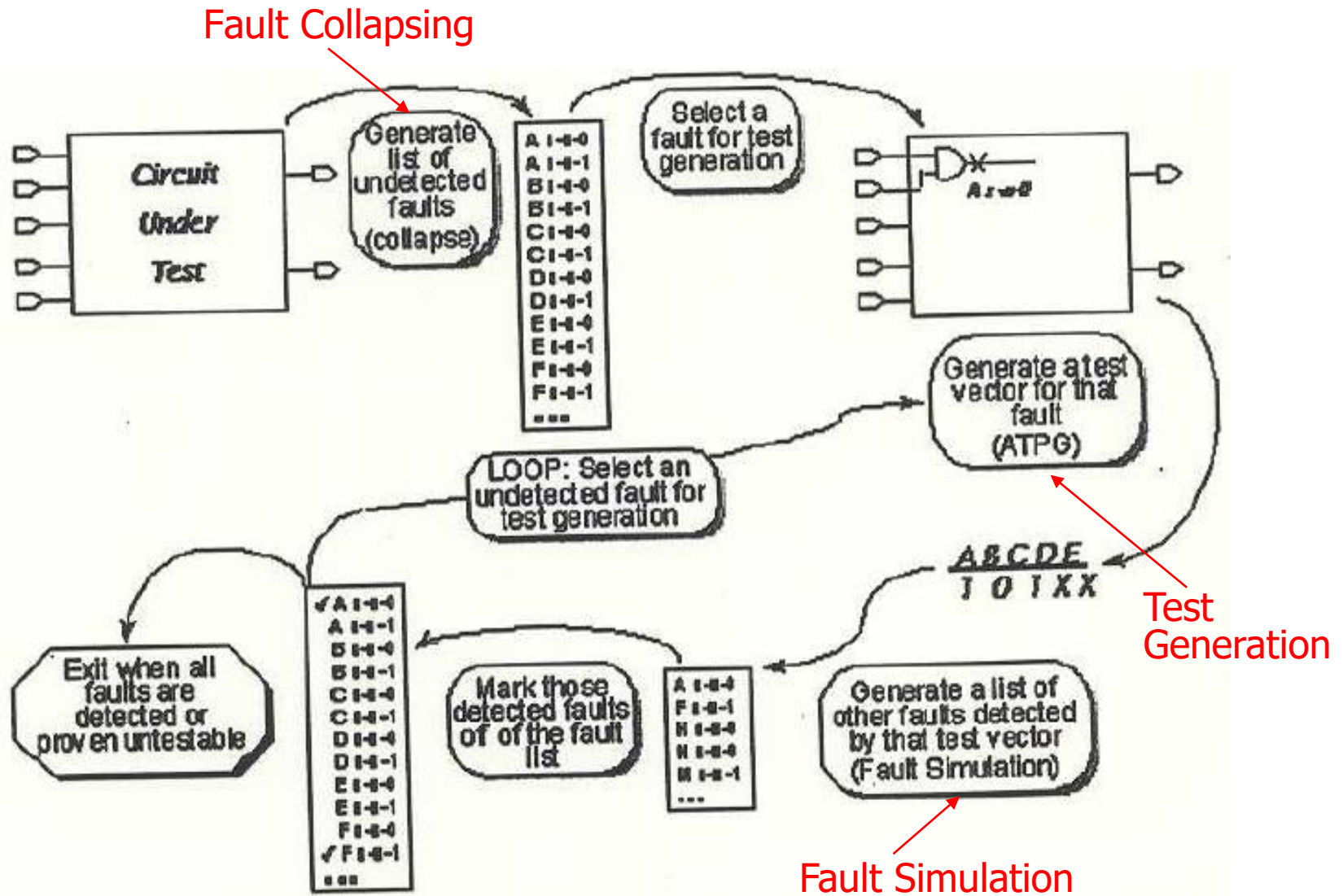

---

# **Fault Collapsing**

# Definitions

---

- Let  $Z(x)$  be the logic function of a combinatorial logic circuit where  $x$  is a specific input vector  $x$
- Let  $Z_f(x)$  be the logic function of a combinatorial logic circuit with the fault  $f$  present where  $x$  is a specific input vector  $x$










# Definitions

---

- Circuit is tested by applying a sequence  $T$  of test vectors  $\{t_1, t_2, \dots, t_m\}$  and  
Comparing output response with expected output response  $Z(t_1), Z(t_2), \dots, Z(t_m)$ .
- A test vector  $t$  detects a fault  $f$  iff
$$Z_f(t) \neq Z(t)$$

# Switching Characteristics


- AND, NAND, OR, NOR gates

       

# Switching Characteristics

---


- XOR, XNOR gates

 

# Example Circuit

---


- $Z = (x_2 + x_3) x_1 + x_1' x_4$

 
 
## Example Circuit : $f = x_4 \text{ s-a-0}$

---

- $Z = (x_2 + x_3) x_1 + x_1' x_4$   
becomes
- $Z_f = (x_2 + x_3) x_1$



# Fault Detection

---

- For single-output circuits, a test that detects fault  $f$  makes

$$Z(t) = 0 \text{ and } Z_f(t) = 1$$

or

$$Z(t) = 1 \text{ and } Z_f(t) = 0$$


- Thus the set of all tests that detect  $f$  is given by solutions to

$$Z(x) \oplus Z_f(x) = 1$$
 
## Example Circuit : $f = x_4 \text{ s-a-0}$

---


- $Z = (x_2 + x_3) x_1 + x_1' x_4$   
becomes
- $Z_f = (x_2 + x_3) x_1$


 
## Example Circuit : $f = x_4$ s-a-0

---

- $Z(x) \oplus Z_f(x) = 1$
- $(x_2 + x_3) x_1 + x_1' x_4 \oplus (x_2 + x_3) x_1 = 1$
- $\Rightarrow x_1' x_4$





## Example Circuit : $f = x_4$ s-a-0

- $Z(x) \oplus Z_f(x) = 1$
- $(x_2 + x_3) x_1 + x_1' x_4 \oplus (x_2 + x_3) x_1 = 1$
- $\Rightarrow x_1' x_4$

Means vectors  $(x_4, x_3, x_2, x_1)$


1000

1100

1010

1110

all detect f

 

# Fault Sensitization


---

- A test  $t$  that detects a fault  $f$  activates or generates an error (or fault effect) by creating different Boolean values at site of fault.
- A test  $t$  propagates the error to primary output along a path known as **fault propagation**
- A line whose value in the test  $t$  changes the presence of the fault  $f$  is said to be **sensitized** to the fault  $f$  by test  $t$ .
- The resulting path is said to be the **sensitized path**.

## **f = G2 s-a-1**

---

- Sensitized path: (G2, G4, G5)

 

# Fault Equivalence

---

- Two faults  $f$  and  $g$  are functionally equivalent iff  $z_f(t) = z_g(t)$  under any test set  $T$  ( $t \in T$ ).
- Test (vector)  $t$  distinguishes between two faults  $f$  and  $g$  if  $z_f(t) \neq z_g(t)$  (i.e.  $z_f(t) \oplus z_g(t) = 1$  for a single-output function).
- Equivalency and distinguishability are defined for the faults of the same nature (fault-universe).

# Stuck-at-fault Notation

---

- We will denote stuck-at-faults using dots as a shorthand
- A s-a-1 fault is a black dot •
- A s-a-0 fault is a open circle ◦


# Fault Equivalence Example

---

- NAND-2 gate:

- s-a-1: •

- s-a-0: ○

 

The uncollapsed state has 6 stuck-at-faults

- For the NAND-2 gate:

- The s-a-0 @ x is equivalent to the s-a-0 @ y which is also equivalent to the s-a-1 @ z


- Test pattern  $xy=11$  can detect all of them.

# Fault Equivalence Example

- NAND-2 gate:


- s-a-1: •

- s-a-0: ○

 

The uncollapsed state has 6 stuck-at-faults

 - We can show the collapsed state where we remove equivalent faults (remove input faults) as



The collapsed state has 4 stuck-at-faults

# Controlling and Non-controlling Value

---

- Controlling value : when it present on at least one input of a gate, it forces the output to a known value
  - AND gate, NAND gate : 0
  - OR gate, NOR gate : 1
- Non-controlling value : the complement of the controlling value or (sensitizing value)
  - AND gate, NAND gate : 1
  - OR gate, NOR gate : 0




# Fault Equivalence

---


- In general, for a gate with controlling value  $c$  and inversion  $i$ , all input s-a- $c$  faults and the output s-a- $(c \oplus i)$  fault are functionally equivalent.
- For NAND gate, controlling value  $c$  is 0 and inversion is 1, so input stuck-at-zero faults are equivalent to the output stuck-at-one fault

## Another Example: Or Gate

---

 

 - For an OR gate, controlling value  $c$  is 1 and inversion is 0, so all input s-a-1 is equivalent to output s-a-1
- Test pattern 00 will find all of these faults




Equivalent collapsed faults
 
# Fault Dominance

---

- Let  $T_f$  and  $T_g$  be the set of all tests that detect fault  $f$  and  $g$ , respectively. These are equivalent statements:
  - Fault  $f$  dominates  $g$  (  $g \subseteq f$  )
  - $f$  and  $g$  are functionally equivalent under  $T_g$
  - $T_g \subseteq T_f$
  - Any test that detects  $g$ , i.e.  $z_g(t) \neq z(t)$  will also detect  $f$  on the same primary output because  $z_f(t) = z_g(t)$
- To reduce efforts in testing we can identify and remove the dominating faults (such as  $f$ ) from the set of faults.




# Fault Dominance

---

- In general, for a gate with controlling value  $c$  and inversion  $i$ , the output s-a- $(\bar{c} \oplus i)$  fault dominates any s-a- $\bar{c}$  input fault equivalent.
- For NAND gate, controlling value  $c$  is 0 and inversion is 1, so the output s-a-0 fault dominates the s-a-1 input faults


# Fault Dominance (cont'd)

- Example:

 






 
# Fault Dominance

- In general, for a gate with controlling value  $c$  and inversion  $i$ , the output s-a- $(\bar{c} \oplus i)$  fault dominates any s-a- $\bar{c}$  input fault equivalent.
- For OR gate, controlling value  $c$  is 1 and inversion is 0, so the output s-a-0 fault dominates the s-a-0 input faults



      
# Summary of Equivalent/Dominant Faults

- Equivalence – dashed lines
- Dominance – red lines


 
# Caution in Fault Collapsing

- Try to work on faults in one direction. For example, start from the output gate, apply both equivalency and dominance to the gate and remove as many faults as possible in the output (keep the rest in the input) before going to the next level.
- If you work on both directions when removing fault, some equivalency/dominance may not be seen.
- Example (consider only fault equivalence):






 
# IEEE Gate Symbols

---


- In some of the examples, the standard IEEE symbols of the logic gates will be used




NOT

 

AND

 


NAND

 

OR



XOR

 


NOR




XNOR
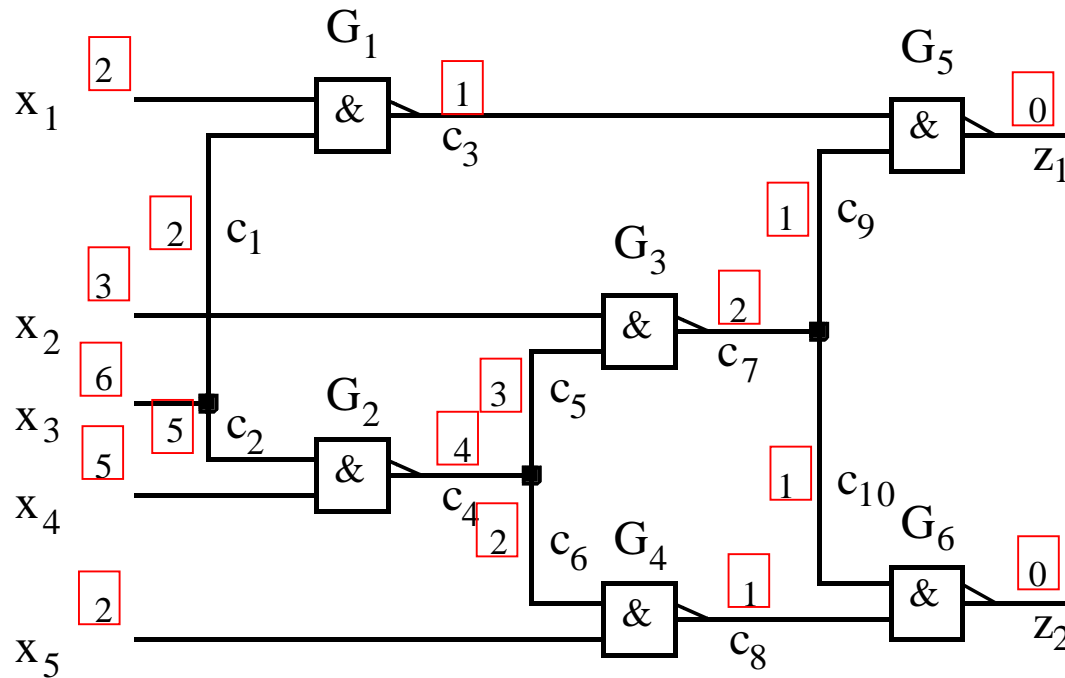
# Fault Collapsing (Dropping) – An Example



- Circuit lines ordered in non-decreasing order of their output level values as  $\{z_2, z_1, c_{10}, c_9, c_8, c_7, c_6, c_5, c_4, c_3, c_2, c_1, x_5, x_4, x_3, x_2, x_1\}$

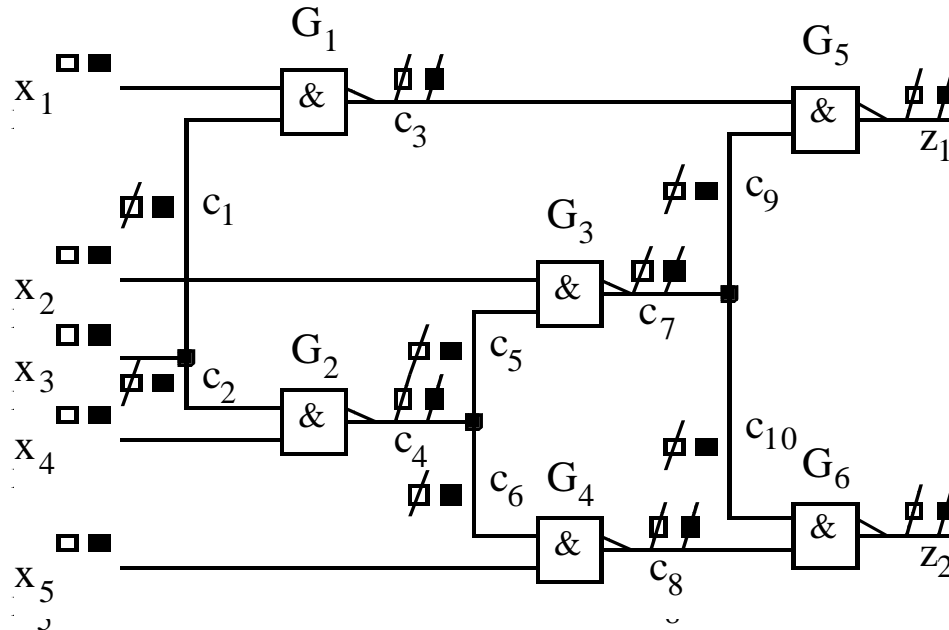
# Fault Collapsing (Dropping) – An Example



- Circuit lines ordered in non-decreasing order of their output level values as  $\{z_2, z_1, c_{10}, c_9, c_8, c_7, c_6, c_5, c_4, c_3, c_2, c_1, x_5, x_4, x_3, x_2, x_1\}$
- Collapse Ratio =  $N_{\text{remaining faults}} / N_{\text{all faults}} = 16/34 = 0.47$
- Note: Faults remain only at primary inputs and fanout branches (Why?)
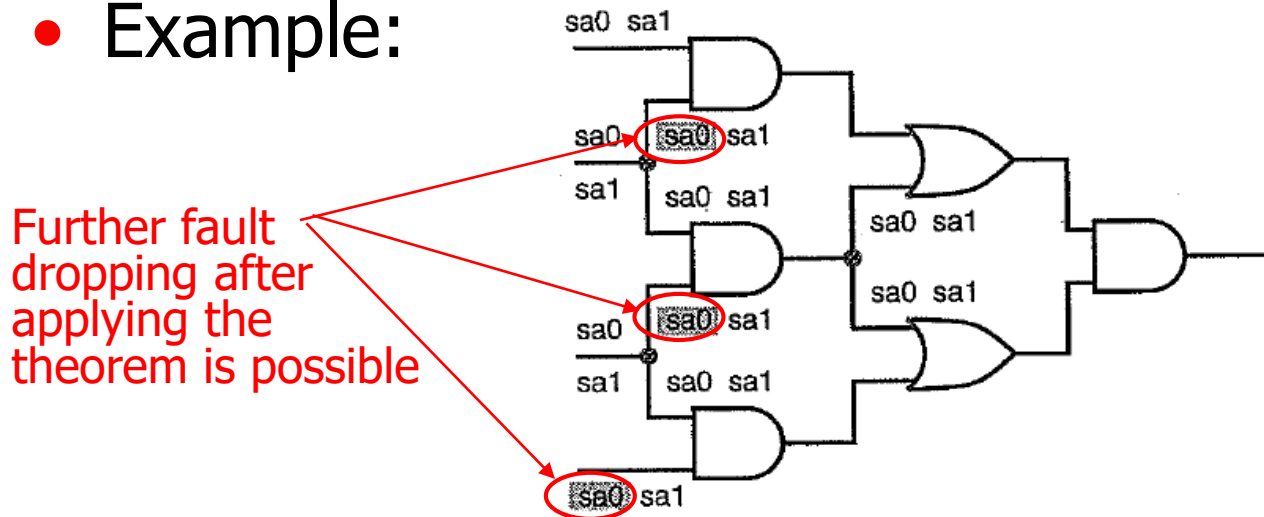
# Checkpoint Theorem

- Definition: Primary inputs and fanout branches of a combinational circuit are called **checkpoints**.
- A test set that detects all single stuck-at faults **at the checkpoints** of a combinational circuit detects all single stuck-at faults in that circuit.
- Example:




Collapse ratio =  $17/32 = 0.53$

- Proof: By contradiction.

---

# **Test Generation**

# Fault Analysis System (Review)

 

# Test Generation Techniques

---

- There are two main test vector generation techniques

## 1. Non-Structural

- Analyzes the gate-level description of a circuit and implicitly enumerate all possible input combinations to find a test vector for a target fault.

## 2. Structural

- Analyzes the structure of a given circuit to generate a test vector for a given target fault, or declare it untestable.


---

# **Non-Structural Test Generation**


 
# Fault Detection in Combinational Circuits

- A test (vector)  $t$  detects a fault  $f$  if and only if  $Z_f(t) \neq Z(t)$  (i.e., at least one of the outputs are different in  $N$  and  $N_f$ ).
- For a single output circuit  $Z_f(t) \neq Z(t)$  is equivalent to  $Z_f(t) \oplus Z(t) = 1$
- Example: find tests to detect s-a-0 at  $x_4$ .



## **Fault Detection in Combinational Circuits (cont'd)**

- Fault-free output:  $Z = (x_2 + x_3) \cdot x_1 + \bar{x}_1 \cdot x_4$
- Faulty output:  $Z_f = (x_2 + x_3) \cdot x_1$
- $Z \oplus Z_f = [(x_2 + x_3) \cdot x_1 + \bar{x}_1 \cdot x_4] \oplus [(x_2 + x_3) \cdot x_1] = \dots = \bar{x}_1 \cdot x_4$
- Test vectors to detect s-a-0 at  $x_4$  satisfy  $\bar{x}_1 x_4 = 1$  that are:

$x_1$	$x_2$	$x_3$	$x_4$	$\equiv$	$x_1$	$x_2$	$x_3$	$x_4$
0	x	x	1		0	0	0	1
					0	0	1	1
					0	1	0	1
					0	1	1	1

# Boolean Difference

---

- Consider a Boolean function  $f(x)$  where  $x=(x_1,x_2,\dots,x_i,\dots,x_n)$  is the input vector.

- Cofactors of  $f$ :
$$\begin{cases} f_{x_i} = f|_{x_i=1} = f(x_1,\dots,x_i=1,\dots,x_n) \\ f_{\bar{x}_i} = f|_{x_i=0} = f(x_1,\dots,x_i=0,\dots,x_n) \end{cases}$$

- Shannon Expansion Theorem:

$$\begin{cases} f(x) = x_i \cdot f_{x_i} + \bar{x}_i \cdot f_{\bar{x}_i} \\ f(x) = (x_i + f_{\bar{x}_i}) \cdot (\bar{x}_i + f_{x_i}) \end{cases}$$

# Boolean Difference (cont'd)

---

- Definition of Boolean difference:

$$\frac{df}{dx_i} = f_{x_i} \oplus f_{\bar{x}_i}$$


- $\frac{df}{dx_i} = 0$  means s-a-0 or s-a-1 at  $x_i$  cannot be observed at the output. In other words, s-a-f at  $x_i$  is undetectable.
- If  $\frac{df}{dx_i} = 1$  then:
  - $\frac{df}{dx_i} \cdot x_i = 1$  gives all test vectors that can detect s - a - 0 at  $x_i$
  - $\frac{df}{dx_i} \cdot \bar{x}_i = 1$  gives all test vectors that can detect s - a - 1 at  $x_i$

Propagate the fault effect

Stimulate the fault

## Boolean Difference (cont'd)

- Example:

 

$$f = \overline{a}b \cdot (a + p)$$

$$\frac{df}{dp} = f|_{p=0} \oplus f|_{p=1} = [\overline{a}b \cdot a] \oplus [\overline{a}b] = [(ab + \overline{a}) \cdot \overline{a}b] + (\overline{a}b \cdot a) \cdot ab$$

$$= ab \cdot \overline{a}b + (\overline{a} \cdot \overline{a}b) = \overline{a} \cdot (\overline{a} + b) = \overline{a}$$

$$\Rightarrow \frac{df}{dp} \cdot p = \overline{a} \cdot b = 1 \Rightarrow ab = 01$$


- So  $ab=01$  is the only test vector that can detect s-a-0 at line p.

---

# **Structural Test Generation**

# Motivation

- Consider a 64-bit ripple-carry adder

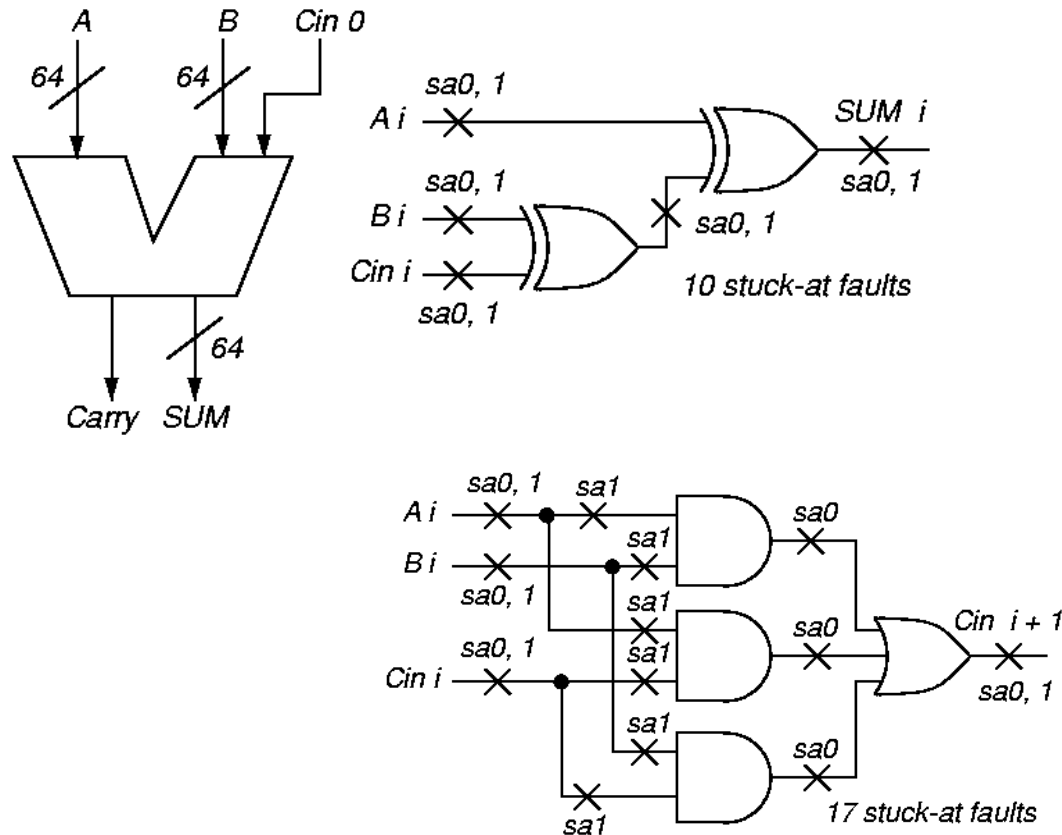

## Motivation (cont.)

---

- Functional (exhaustive) ATPG – generate complete set of tests for circuit input-output combinations
  - 129 inputs, 65 outputs:
  - $2^{129} = 680,564,733,841,876,926,926,749,214,863,536,422,912$  patterns
  - Using 1 GHz ATE, would take  $2.15 \times 10^{22}$  years
- Structural test:
  - No redundant adder hardware, 64 bit slices
  - Each with 27 faults (using fault equivalence)
  - At most  $64 \times 27 = 1728$  faults (tests)
  - Takes  $0.000001728$  s on 1 GHz ATE
- Designer gives small set of functional tests – augment with structural tests to boost coverage to 98+ %






# Algebra for Structural Test

---

- Represent two machines, which are simulated simultaneously by a computer program:
  - Good circuit machine (1<sup>st</sup> value)
  - Bad circuit machine (2<sup>nd</sup> value)
- Better to represent both in the algebra:
  - Need only 1 pass of ATPG to solve both
  - Good machine values that preclude bad machine values become obvious sooner & vice versa
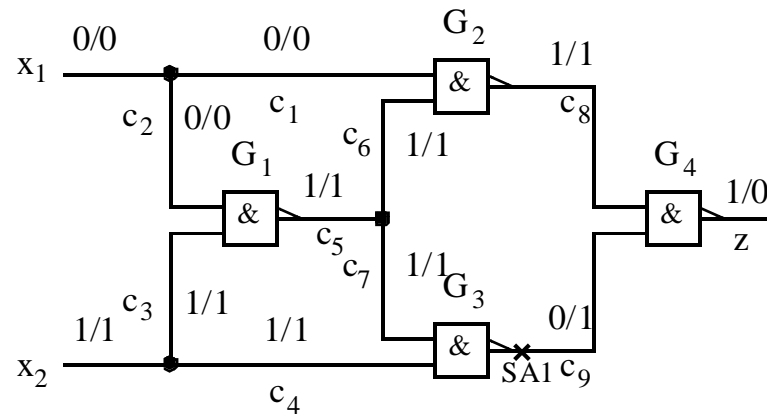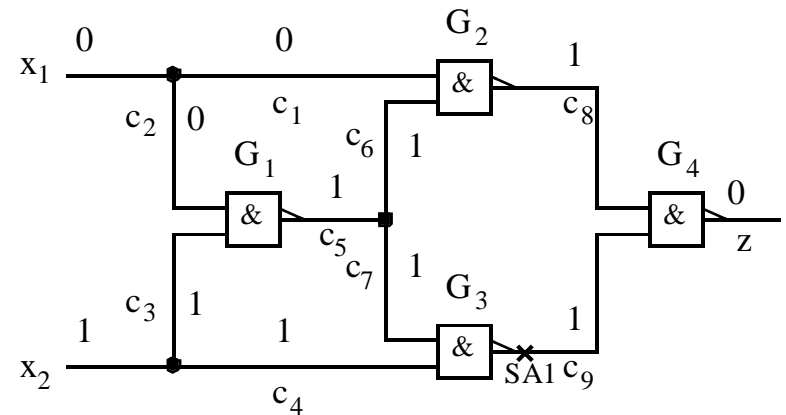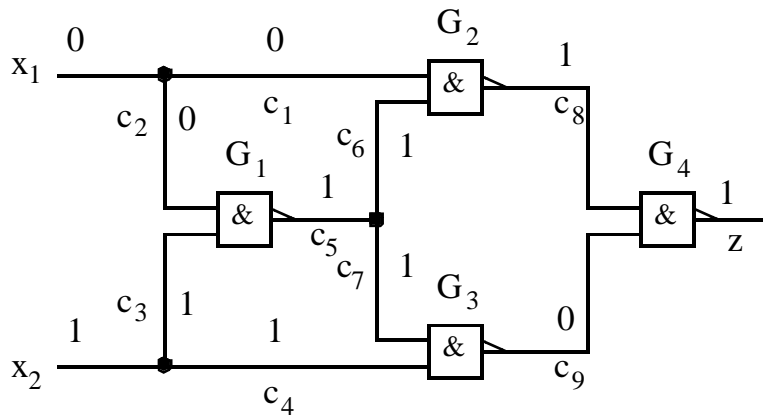
# Circuit Representation

- It's more efficient to carry (simulate) fault-free and faulty values at the same time.



# Algebra for Structural Test (cont.)

- Roth's 5-Valued and Muth's 9-Valued Algebra

Symbol	Meaning	Fault-Free (Good)	Faulty (Bad)
0	0/0	0	0
1	1/1	1	1
D	1/0	1	0
$\overline{D}$	0/1	0	1
X	X/X	X	X
G0	0/X	0	X
G1	1/X	1	X
F0	X/0	X	0
F1	X/1	X	1

5-Valued


9-Valued

# Operations in Multi-Valued Logic

- Examples (2-input AND and OR gates)

AND	0	1	$D$	$\bar{D}$	$x$
0	0	0	0	0	0
1	0	1	$D$	$\bar{D}$	$x$
$D$	0	$D$	$D$	0	$x$
$\bar{D}$	0	$\bar{D}$	0	$\bar{D}$	$x$
$x$	0	$x$	$x$	$x$	$x$

OR	0	1	$D$	$\bar{D}$	$x$
0	0	1	$D$	$\bar{D}$	$x$
1	1	1	1	1	1
$D$	$D$	1	$D$	1	$x$
$\bar{D}$	$\bar{D}$	1	1	$\bar{D}$	$x$
$x$	$x$	1	$x$	$x$	$x$


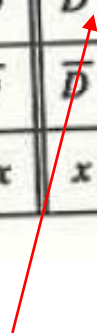


- e.g.  $D+0=1/0+0/0=1/0=D$

# Path Sensitization

- Three key tasks are needed
  1. Fault Sensitization (Stimulation)
  2. Fault (Effect) Propagation
  3. Line Justification
- Forward and Backward Implications


Examples of  
Forward  
Implications

  

Examples of Backward  
Implications


# Path Sensitization Example

- Propagate through top path

 
 
## Path Sensitization Example (cont.)


- Propagate through top and bottom paths simultaneously



## Path Sensitization Example (cont.)

- Propagate through the bottom path simultaneously

**Test Pattern Found**

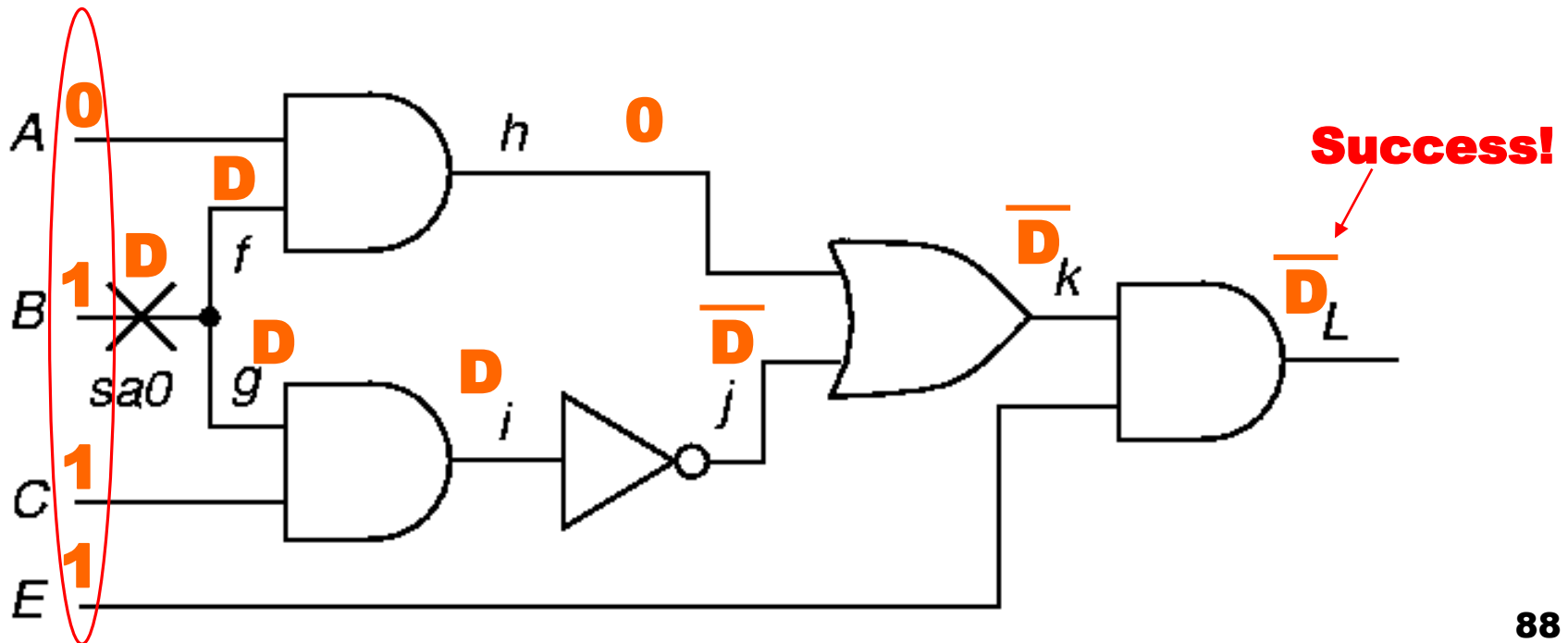



# D-Algorithm

---

- Initialization
- Identification of test generation sub-tasks (TGSTs)
  0. If impossible, BACKTRACK; if complete, STOP
  1. Fault-effect excitation (FEE) – **necessary**
  2. Fault-effect propagation (FEP)
    - Each gate in D-frontier D an **alternative**
  3. Justification
    - Every gate in unjustified set U – **necessary**
- Select a TGST
  - Identify local value assignment for selected TGST
    - FEE – values at **outputs** of faulty circuit element
    - FEP – value at the **output** of gate selected for FEP
    - Justification – values at **inputs** of gate selected for justification

## D-Algorithm (cont.)

---

- Value assignment
  - Store untried alternative TGSTs and untried alternative value assignment for selected TGST
  - Store the values at all circuit lines
  - Make selected local value assignment (VA)
  - Perform implication – if CONFLICT, then BACKTRACK
- BACKTRACK
  - Find most recently selected VA or TGST for which one (or more) untried alternative exists
  - Restore values to **before** above assignment was made
  - Select an untried alternative TGST and/or untried local VA and repeat the value assignment step

# History of Algorithms


---

Algorithm	Est. speedup over D-ALG (normalized to D-ALG time)	Year
<b>D-ALG</b>	<b>1</b>	<b>1966</b>
<b>PODEM</b>	<b>7</b>	<b>1981</b>
<b>FAN</b>	<b>23</b>	<b>1983</b>
<b>TOPS</b>	<b>292</b>	<b>1987</b>
<b>SOCRATES</b>	<b>1574 † ATPG System</b>	<b>1988</b>
<b>Waicukauski et al.</b>	<b>2189 † ATPG System</b>	<b>1990</b>
<b>EST</b>	<b>8765 † ATPG System</b>	<b>1991</b>
<b>TRAN</b>	<b>3005 † ATPG System</b>	<b>1993</b>
<b>Recursive learning</b>	<b>485</b>	<b>1995</b>
<b>Tafertshofer et al.</b>	<b>25057</b>	<b>1997</b>

---

# **Fault Simulation**

# Fault Analysis System (Review)

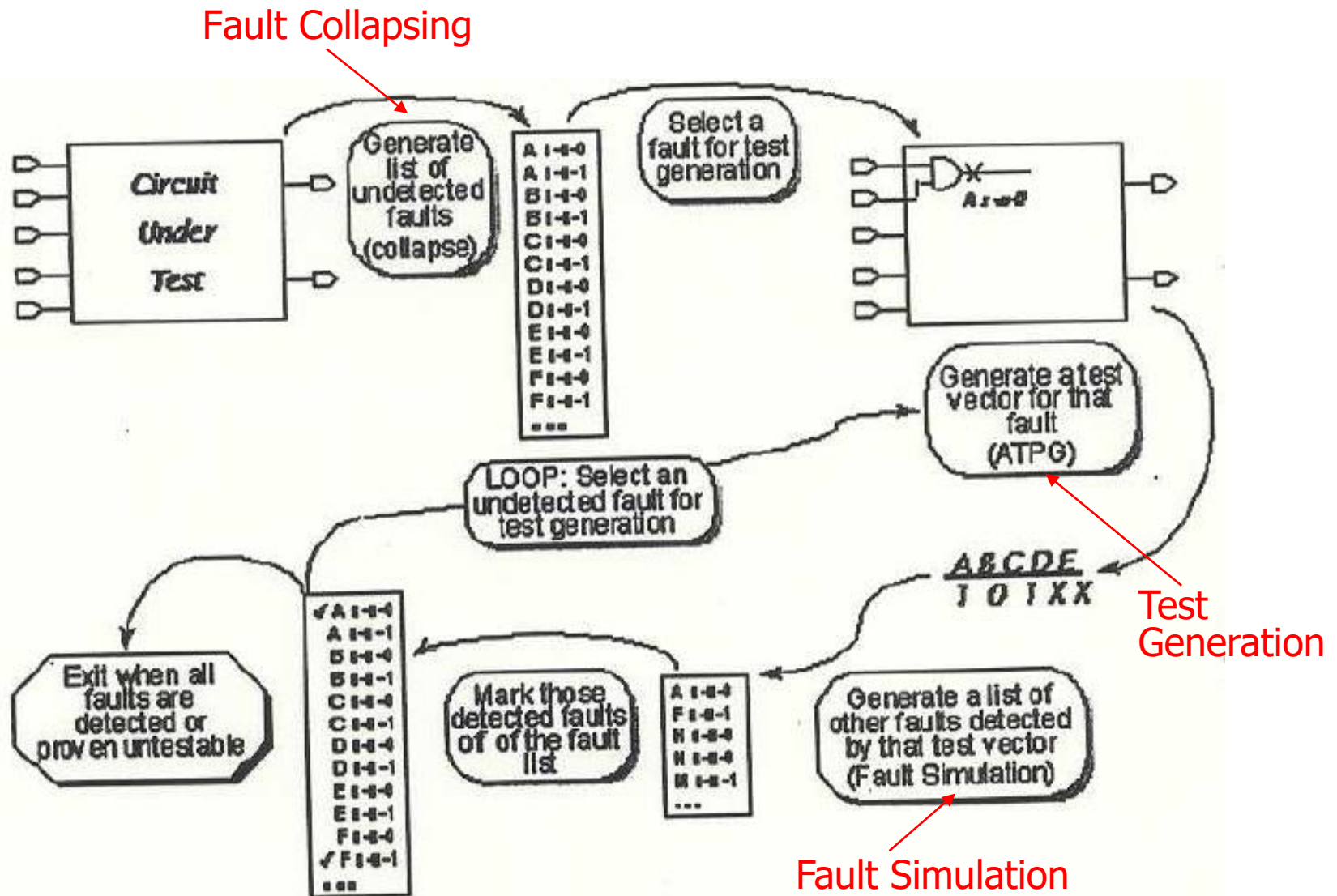


# **Why Fault Simulation?**

---

- 1. To evaluate the quality of a test set**
  - usually in terms of fault coverage**
- 2. To incorporate into ATPG for test generation**
  - due to its lower complexity**
- 3. To construct fault dictionary**
  - for post-test diagnosis**

# Conceptual Fault Simulation

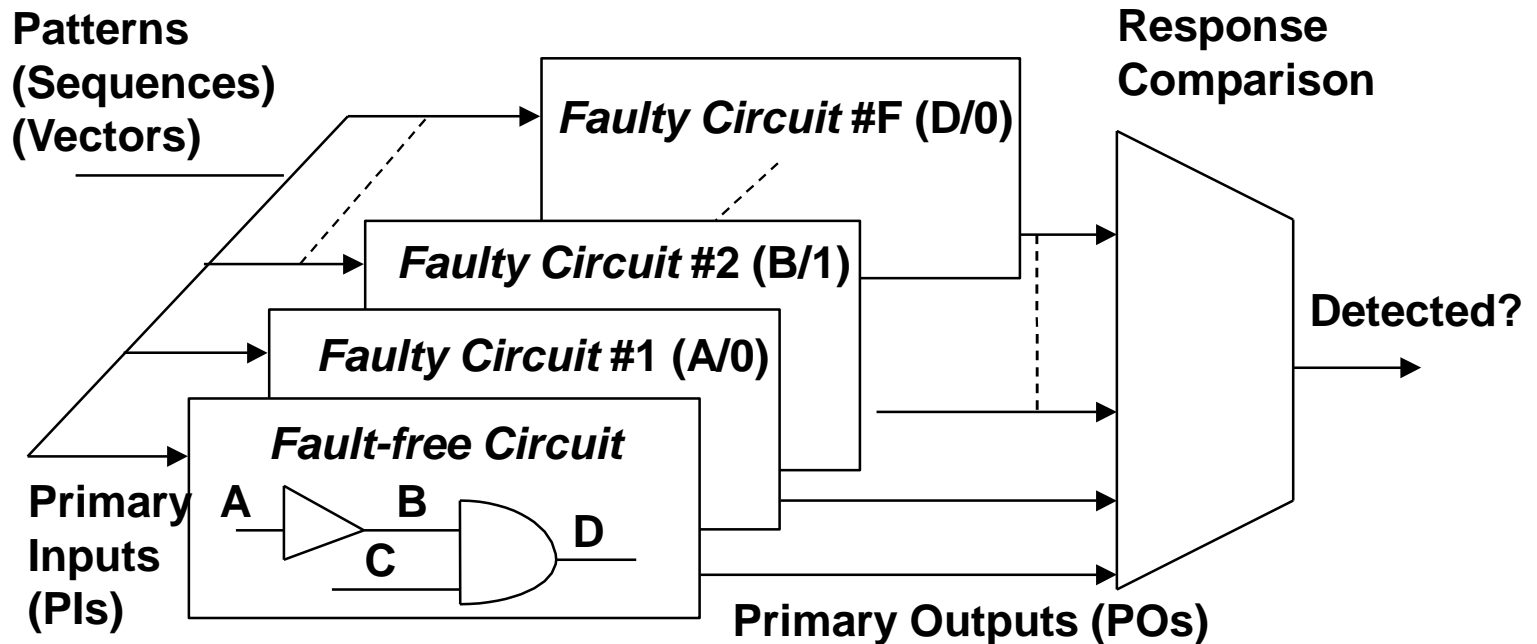

- Logic simulation on both good (fault-free) and faulty circuits

---


# Some Basics for Logic Simulation

- For fault simulation purpose, mostly the gate delay is assumed to be zero unless the delay faults are considered. Our main concern is the functional faults.
- The logic values can be either two (0, 1) or three values (0, 1, X). For delay fault, more values will be needed.
- Two simulation mechanisms:
  - Oblivious compiled-code: circuit is translated into program and all gates are executed for each pattern.
  - Interpretive event-driven: circuit structure and gate status are stored in the table and only those gates needed to be updated with a new pattern are processed.



# Oblivious Compiled Code

---

 

- **Compiled codes**


- **LDA**     **A**     */\* load accumulator with value of A \*/*
- **AND**     **B**     */\* calculate A and B \*/*
- **AND**     **C**     */\* calculate E = AB and C \*/*
- **OR**      **D**     */\* calculate Z = E or D \*/*
- **STA**     **Z**     */\* store result of Z \*/*

# Event-Driven

---

- **While (event list not empty) begin**
  - **$t$  = next time in the list**
  - **for every event  $(i, t)$  begin**
    - **update value of gate  $i$**
    - **schedule fanout gates of  $i$  in the event list if value changes are expected**
  - **end**
- **end**

# Complexity of Fault Simulation

 


- **Complexity =  $P * F * G \sim O(G^3)$  with single s-a faults**
- **The complexity is higher than logic simulation,  $O(G^2)$ , but is much lower than test pattern generation.**
- **In reality, the complexity is much lower due to fault dropping and advanced techniques.**
 
# Characteristics of Fault Simulation

---

- Fault activity with respect to fault-free circuit is often sparse both in time and in space.
- For example, F1 is not activated by the given pattern, while F2 affects only the lower part of this circuit.



- The efficiency of a fault simulator depends on its ability to exploit these characteristics.

# Fault Simulation

---

- **Goal:** to determine the list of faults in a CUT (Circuit Under Test) and to simulate the fault-free and faulty circuits efficiently to determine if their outputs are different
- Methodologies
  - Parallel
  - Deductive
  - Concurrent
  - Critical Path Tracing

# Classical Fault Simulation Techniques

---

- **Common Characteristics:**
  - In general, no restriction on the circuit types.
  - Developed before VLSI era.
- **Serial Fault Simulation**
  - trivial single-fault single-pattern
- **Parallel Fault Simulation**
- **Deductive Fault Simulation**
- **Concurrent Fault Simulation**

# Parallel Fault Simulation

---

- **Taking advantage of inherent parallel operation of computer words to simulate faulty circuits in parallel with fault-free circuit**
  - the number of faulty circuits, or faults, can be processed parallelly is limited by the word length.
- **Straightforward and memory efficient**
- **Some weaknesses:**
  - An event, a value change, of a single fault or fault-free circuit leads to the computation of the entire word.
  - The fault-free logic simulation is repeated for the number of passes.


# Example of Parallel Fault Simulation

- Consider three faults: B/1, F/0, and J/0

— Bit-space: 

J/0	B/1	F/0	FF
-----	-----	-----	----

 where FF = Fault-free

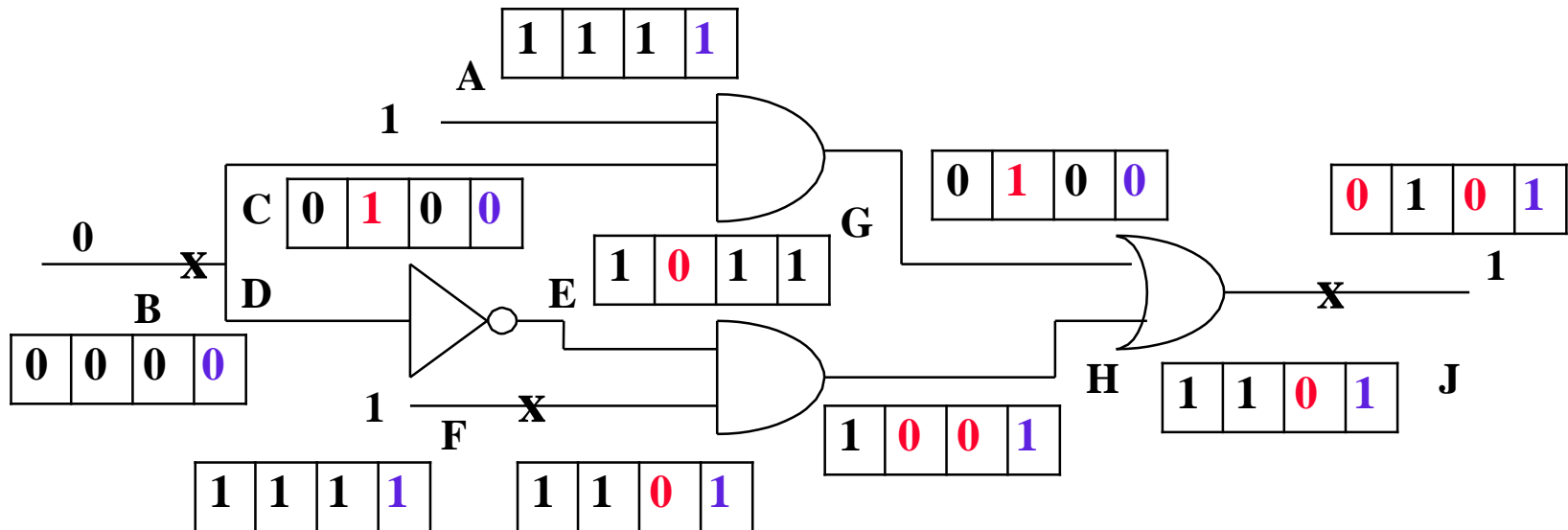



# **Deductive Fault Simulation**

---

- **A list of faults associated with each line containing the identifier of each fault which produces a fault effect on this line.**
  - **Only the faults with fault effect, or difference w.r.t. fault-free circuit, is retained in the list.**
- **The propagation of such lists can be based on set operation derived the gate types and values.**
  - **The list update is performed with each new pattern, which is not efficient.**
  - **The list may dynamically grow its size, which incurs memory explosion problem.**

# Fault List Propagation Rule

---

- Let the gate  $G = F(A,B)$  with input lists  $LA$  and  $LB$  and output list  $LG$  to be updated.
- If in the fault-free circuit,
  - the value of  $G$  is 0(1), use  $F(F-)$
  - the value of gate input  $A$  is 0(1), replace  $A$  in logic expression by  $LA(LA-)$  and  $A-$  by  $LA-(LA)$ .
- Replace  $*$  by *intersection* and  $+$  by *union*.
- Add  $G/1(G/0)$  to the list  $LG$ .

# Fault List Propagation Rule

---

- Let  $I$  be the set of inputs of a gate  $Z$  with controlling value  $c$  and inversion  $i$ . Let  $C$  be the set of inputs with value  $c$ . The fault list of  $Z$  is computed as follows:

$$\text{if } C = \emptyset \text{ then } L_Z = \left\{ \bigcup_{j \in I} L_j \right\} \cup \{Z \text{ s} - a - (c \oplus i)\}$$


$$\text{else } L_Z = \left\{ \bigcap_{j \in I} L_j \right\} - \left\{ \bigcup_{j \in I - C} L_j \right\} \cup \{Z \text{ s} - a - (\bar{c} \oplus i)\}$$

In other words, if no input has value  $c$ , any fault effect on an input propagates to the output. If some inputs have value  $c$ , only a fault effect that affects all the inputs at  $c$  without affecting any of the inputs at  $\bar{c}$  propagates to the output. In both cases we add the local fault of the output.

# Illustration of Fault List Propagation

---

Consider a two-input AND gate

 

**Case 1: A=1, B=1, C=1 at fault-free,**

$$LC = LA + LB + \{C/0\}$$

**Case 2: A=1, B=0, C=0 at fault-free,**

$$LC = LA - * LB + \{C/1\}$$


**Case 3: A=0, B=0, C=0 at fault-free,**

$$LC = LA * LB + \{C/1\}$$

# Example of Deductive Simulation    la

---

- Consider 3 faults: B/1, F/0, and J/0

 


$LB = \{B/1\}, \quad LF = \{F/0\}, \quad LA = 0$

$LC=LD = \{B/1\}$

# Example of Deductive Simulation Ib

- Consider 3 faults: B/1, F/0, and J/0

 


$LB = \{B/1\}, \quad LF = \{F/0\},$

$LC=LD = \{B/1\},$

$LG = \{B/1\}, \quad LE = \{B/1\}$

# Example of Deductive Simulation Ic

- Consider 3 faults: B/1, F/0, and J/0

 


$LB = \{B/1\}, \quad LF = \{F/0\},$   
 $LC=LD = \{B/1\}, \quad LG = \{B/1\},$   
 $LE = \{B/1\}, \quad LH = \{B/1, F/0\}$

# Example of Deductive Simulation Id

---

- Consider 3 faults: B/1, F/0, and J/0

 


$LB = \{B/1\}, \quad LF = \{F/0\},$   
 $LC=LD = \{B/1\}, \quad LG = \{B/1\},$   
 $LE = \{B/1\}, \quad LH = \{B/1, F/0\}, \quad LJ = \{F/0, J/0\}$



# Example of Deductive Simulation II

- When A changes from 1 to 0

 

$LB = \{B/1\}, \quad LF = \{F/0\},$

$LC=LD = \{B/1\}, \quad LG = 0,$


$LE = \{B/1\}, \quad LH = \{B/1, F/0\}, \quad LJ = \{B/1, F/0, J/0\}$

# Concurrent Fault Simulation

---


- Each gate retains a list of fault copies each of which stores the status of a fault exhibiting difference from fault-free values.
- Simulation mechanism is similar to the conceptual fault simulation except that only the dynamical difference w.r.t. fault-free circuit is retained.
- Very versatile in circuit types and gate delays
- Although theoretically all faults in a circuit can be processed in one pass, memory explosion problem restricts the fault number in each pass.

# Concurrent Fault Simulation

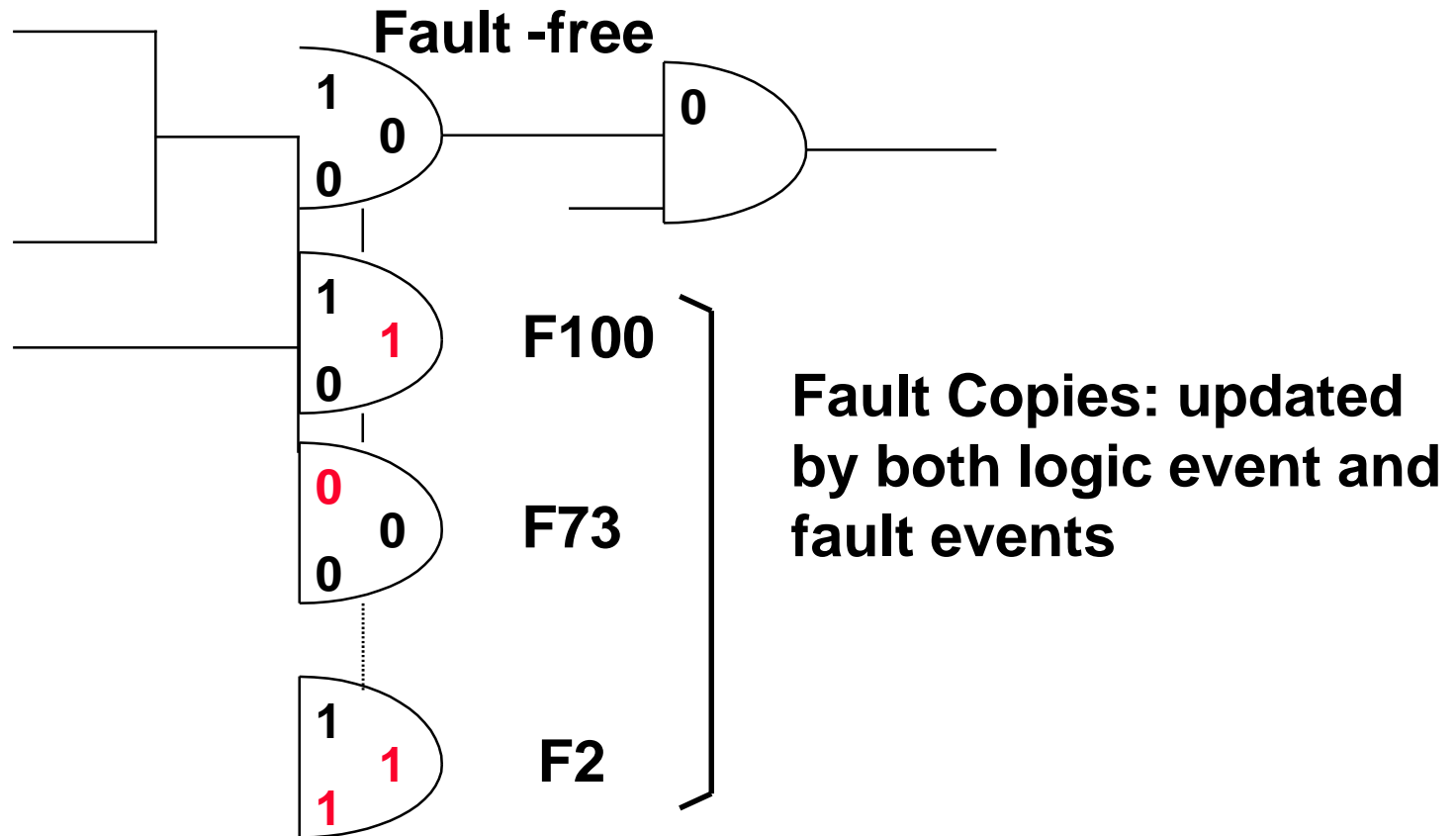

# Example of Concurrent Simulation I

- Consider 3 faults: B/1, F/0, and J/0

 


$LG = \{10\_0, B/1:11\_1\}$       $LE = \{0\_1, B/1:1\_0\}$

$LH = \{11\_1, B/1:01\_0, F/0:10\_0\}$

$LJ = \{01\_1, B/1:10\_1, F/0:00\_0, J/0:01\_0\}$

# Example of Concurrent Simulation II

- When A changes from 1 to 0

 

**LG** = {00\_0, B/1:01\_0}     **LE** = {0\_1, B/1:1\_0}

**LH** = {11\_1, B/1:01\_0, F/0:10\_0}

**LJ** = {01\_1, B/1:00\_0, F/0:00\_0, J/0:01\_0}

# **Modern Combinational Simulation Techniques**

---


- **Parallel pattern**
- **Critical path tracing**
- **Other sophisticated techniques**

# Parallel-Pattern Single-Fault Propagation (PPSFP)

---

- Many patterns are simulated in parallel for both fault-free and faulty circuits. The number of patterns is a multiple of computer word length.
- Coincident logic events of fault-free circuit from these patterns can be simulated in parallel.
  - reduction of logic event simulation time
- Coincident fault events of faulty circuits from these patterns can also be simulated in parallel.
  - reduction of fault event simulation time
- Simple and extremely efficient
  - basis of all modern combinational fault simulators

# Comparison with Parallel-Fault

 

- Fault event maps for parallel-pattern (upper) and parallel-fault (lower)
- **Parallel-Pattern case:**  
Consider three **patterns**: P1, P2, P3.
- **Parallel-Fault case:**  
Consider three **faults**: F1, F2, F3.
- The **overlapping** of fault events is inherently much higher in parallel-pattern simulation, and hence more event can be done at the same time.




# Example of Parallel Pattern Simulation

- Consider one fault **F/0** and four patterns: **P3,P2,P1,P0**

— Bit-space: 

P3	P2	P1	P0
----	----	----	----

 faulty value in **red**

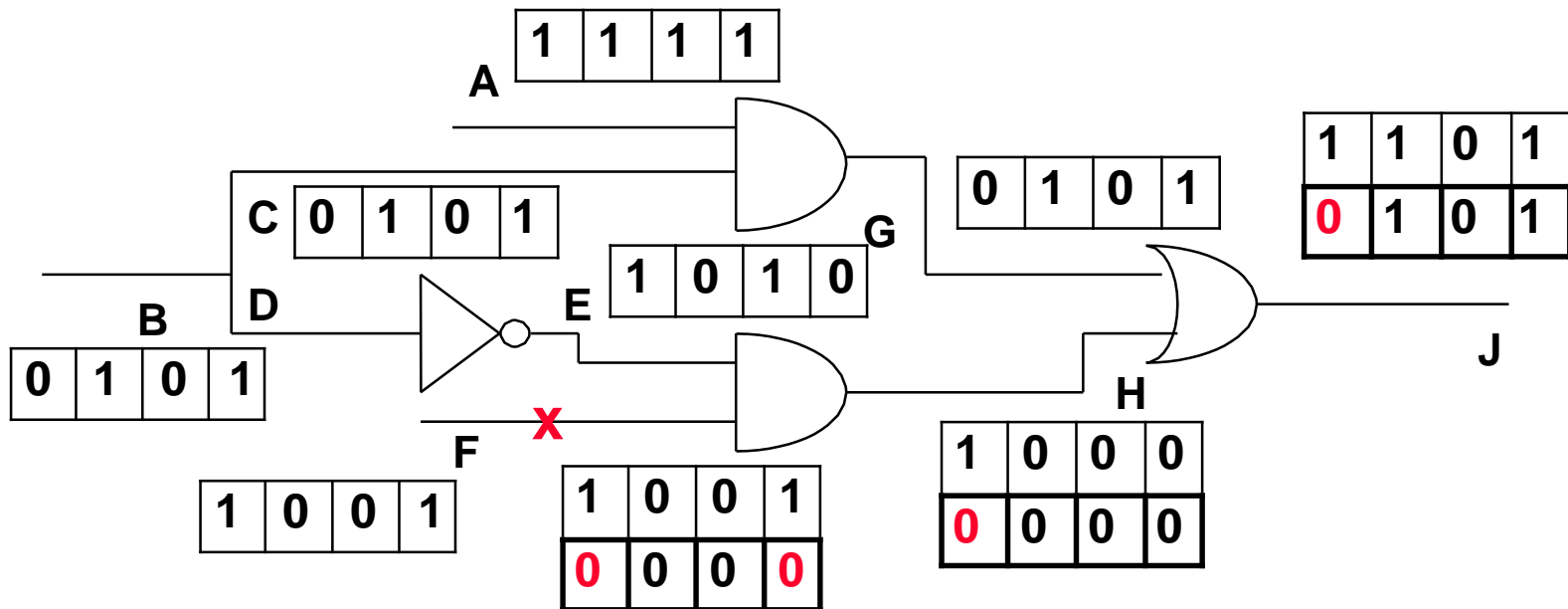

# Critical Path Tracing

---

- **Two-step Procedure:**
  - **Fault-free simulation and identification of the sensitive gate inputs**
  - **Backtracing to identify the critical lines (critical path tracing)**
- **$O(G)$  complexity for fanout-free circuits --- very rare in practice**
- **However, it becomes effective in fanout-free region when stem faults are simulated by parallel-pattern fault simulator.**


# Critical Path Tracing

---

- Efficient since it implicitly targets all faults in a circuit in a single pass
- However, in its basic form applicable only to fanout-free circuits, i.e., circuits with no fanout systems
- Since most practical circuits have fanouts
  - Circuits are partitioned into fanout-free regions
  - Critical path tracing applied within each fanout-free region
  - Additional steps are needed to check criticality of the paths across fanout-free regions (FFR)

# Fanout-Free Circuits

---

 

- **Definition:** (1) Every line branches out to at most one gate (2) There is just one path from every line to the primary output
- **Theorem:** In a fanout-free circuit, every test set that detects all SSL faults on primary input lines is complete.
- **Corollary:** An  $n$ -input fanout-free circuit can be tested with at most  $2n$  test patterns (non-optimal)

# Critical Path Tracing

---


- Efficient since it implicitly targets all faults in a circuit in a single pass
- However, in its basic form applicable only to fanout-free circuits, i.e., circuits with no fanout systems
- Since most practical circuits have fanouts
  - Circuits are partitioned into fanout-free regions
  - Critical path tracing applied within each fanout-free region
  - Additional steps are needed to check criticality of the paths across fanout-free regions (FFR)

# Basics of Critical Path Tracing

---

- A line  $l$  is **critical** w.r.t. a pattern  $t$  iff  $t$  detects the fault  $l/v$ .
- Paths of critical lines are critical paths.
- A gate input  $i$  is *sensitive* if complementing the value of  $i$  changes the value of the gate output.
- A gate input  $i$  is **critical** w.r.t. a pattern  $t$  if the gate output is critical and  $i$  is sensitive w.r.t.  $t$ .
- In a fanout-free circuit, the criticality of all lines can be determined by backward traversing the successive sensitive gate inputs from POs, in linear time.


# Example of Critical Path Tracing

 

Detected faults in the fanout-free region:  
 $\{J/0, H/0, F/0, E/0, D/1\}$
 
# Anomaly of Critical Path Tracing

- Stem criticality is hard to infer from branches.  
E.g. is B/1 detectable by the given pattern?




- It turns out B/1 is not detectable even though both C and D are critical, because its effects cancel each other out at gate J.
- There is also multiple path sensitization problem.



# Multiple Path Sensitization

- sensitive input, — critical line

 

Both C and D are not critical, yet B is critical and B/0 can be detected at J by multiple path sensitization.


# Key Concept

---

- Given a vector  $P = (p_1, p_2, \dots, p_n)$ , assume fault-free circuit simulation has been performed to compute the value implied at each line by  $P$ 
  - An input  $c_{i_1}$  of a gate  $G$  is said to be **sensitive** at its output  $c_j$ , if complementing the values at  $c_{i_1}$  (without changing values at any of  $G$ 's other inputs) will complement the value at  $c_j$
  - A line  $c_i$  in a circuit  $C$  is said to be **critical** for vector  $P$ , if  $P$  detects a SA $\overline{\alpha}$  Fault at  $c_i$ , when  $P$  implies a value  $w$  at  $c_i$

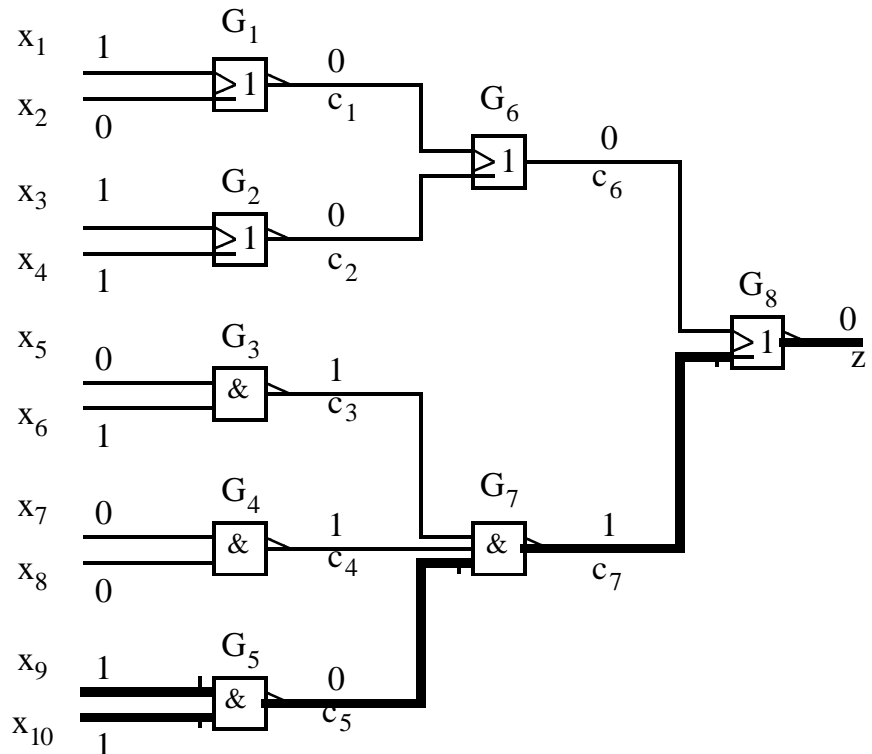
# Critical Path Tracing - Process

- Perform fault-free circuit simulation
- Compute sensitivity of each input of each gate
- Mark the output as critical
  - Traversing the circuit lines from output to inputs, compute criticality of each line



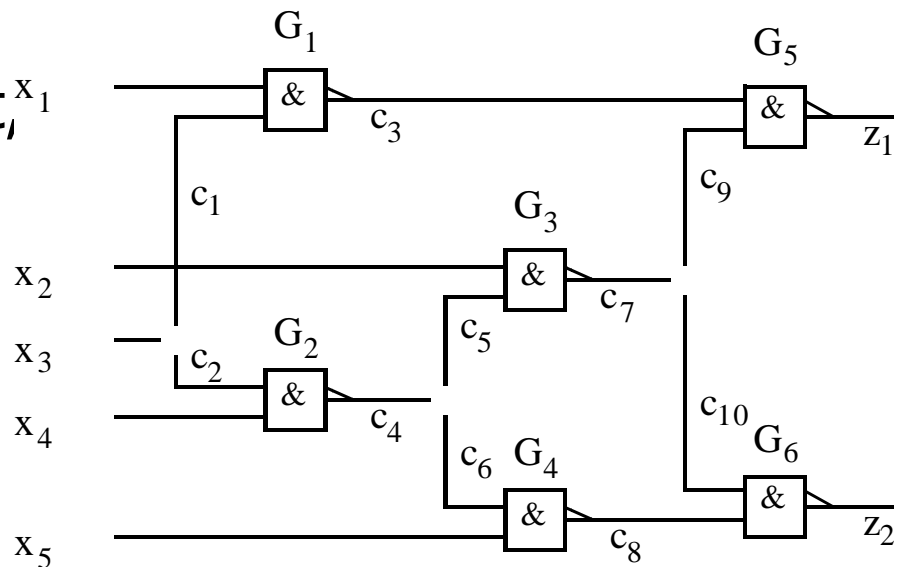
# Critical Path Tracing – Process (cont'd)

- A circuit with fanouts can be partitioned into **fanout-free regions** (FFRs) by disconnecting each stem from its branches
  - Each connected sub-circuit is an FFR
  - Each FFR can be identified by its output, which is either a primary output or a stem of a fanout system
  - Hence, we will refer to an FFR by its output,  $x_1$  as  $\text{FFR}(x_3)$ ,  $\text{FFR}(c_4)$ ,  $\text{FFR}(c_7)$ ,  $\text{FFR}(z_1)$ , and  $\text{FFR}(z_2)$


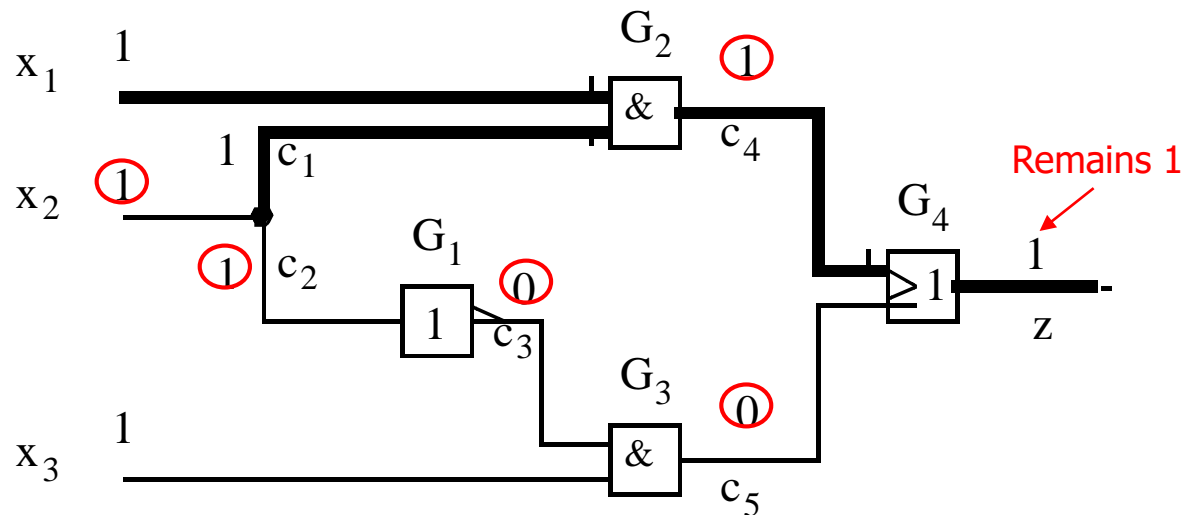
# Critical Path Tracing – Process (cont'd)


- Difficulty with applying critical path tracing to circuits with fanouts
  - This circuit can be partitioned into two FFRs: FFR( $z$ ) and FFR( $x_2$ )



- Critical path tracing on FFR( $z$ ) for this vector identifies  $x_1$ ,  $c_1$ ,  $c_4$ , and  $z$  as critical
- Even though  $c_1$  is critical, explicit fault simulation shows that **the stem  $x_2$  is not critical**
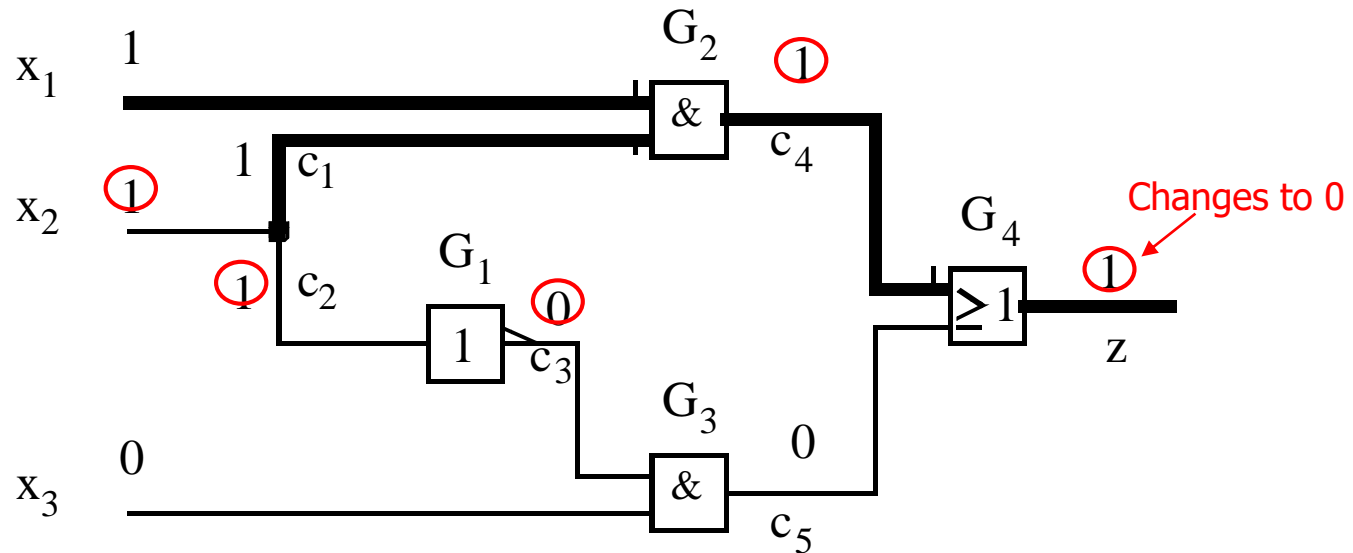
## Critical Path Tracing (cont'd)

- For this vector, critical path tracing of FFR(z) again identifies  $x_1$ ,  $c_1$ ,  $c_4$ , and  $z$  as critical




- However, in this case, **the stem  $x_2$  is critical**
- Hence, no simple universally applicable relation exists between criticality of a stem and those of its branches

## Critical Path Tracing (cont'd)

---

- Above examples show that no universally applicable relation exists between the criticality of a stem and those of its branches
- To obtain a complete fault simulation
  - Critical path tracing can be used within each FFR
  - Explicit fault simulation must be performed for faults at a stem to determine its criticality
  - The results of above two steps can be combined to compute the criticality of all lines in an arbitrary circuit

# Other Sophisticated Techniques

 

$$d(x) = d((x-y1) d(y1) + d(x-y2) d(y2) + d(x-y3)d(y3))$$

- **Stem Region Methods such as Exit Lines**
  - in the right figure,  $d(x)$  is determined from its exit lines  $y1$ ,  $y2$ , and  $y3$
- **Multiple Packet Simulation**
  - use more memory space to improve speed
- **Selective or Demand-driven Fault-free Simulation**
  - reduce unnecessary fault-free simulation as undetected faults become less



# **Hardware Approaches to Fault Simulation**

---


- **Commercialized Dedicated Accelerators:**
  - **IKOS & ZYCAD**
- **Other Hardware Ideas**
  - **Associative Memory**
  - **Cellular Automata**
  - **Field-Programmable Gate Array**

# Cellular Automata

---

- The cellular automata is a 2D array of very simple processors with interconnection to 4 immediate neighbors. It can be regarded as a massively parallel pipelined computer.
- [CA95] shows both gates and interconnects of a circuit can be mapped into the cellular automata and the CA can execute logic and fault simulation with additional comparison.
- Mainly restricted to combinational circuits.

# Field Programmable Gate Array

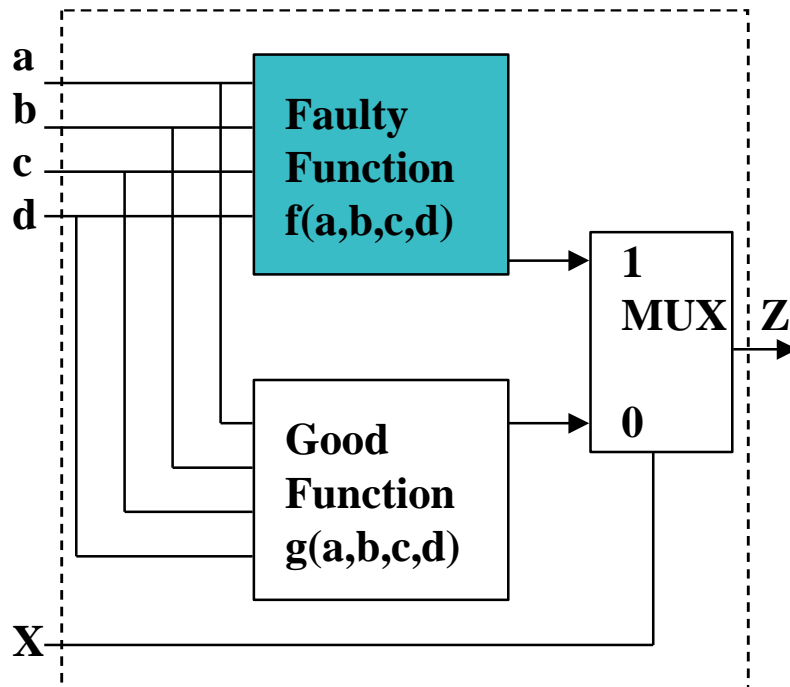

**A CLB with a dynamic fault injected (activated with  $x=1$ )**

Hardware

- **FPGA is a reconfigurable gate array which can be mapped from any logic circuits and emulated much faster than software simulation.**
- **The fault insertion process is slow. One way to minimize the insertion is to have both good gates and faulty gates within FPGA as shown left [FPGA95].**