

---

# EE/CE 6301: Advanced Digital Logic

*Bill Swartz*

**Dept. of EE  
Univ. of Texas at Dallas**

---

# Session 03

## **VHDL-for-Synthesis**

---

# **Dataflow Modeling**


# Dataflow Modeling

- In **Dataflow** style of modeling, the internal working of an entity can be implemented using concurrent signal assignment.
- VHDL code Example:
- Schematics after Synthesis:

```
--Example: 2-1 Mux Dataflow Modeling in VHDL
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;

ENTITY multiplexer2 IS
PORT ( x, y, s : IN  BIT ;
      f : OUT BIT ) ;
END multiplexer2 ;

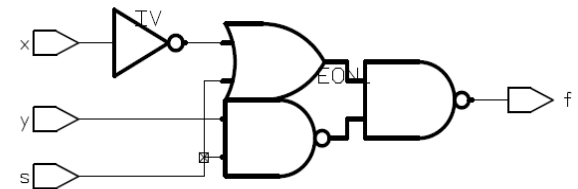ARCHITECTURE multiplexer2_arch OF multiplexer2 IS
BEGIN
f <= (x AND NOT s) OR (y AND s) ;
END multiplexer2_arch ;
```



---

# **Behavioral Modeling**

# Behavioral Description

---

- In **Behavioral** design, we specify the behavior of the circuit, and do not necessarily know the gate level implementation.
- The internal working of an entity can be implemented using a set of statements
- Synthesis takes care of implementing the circuit in gate level
- May or may not produce the most optimized circuit after synthesis

## Example 2: Behavioral 2-1 Mux

---

- VHDL Code:

```
--Example 2: Mux2 Behavioral VHDL code
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity behmux2 is

port ( x, y, s      : in   std_logic ;



      f              : out  std_logic ) ;
end behmux2;

architecture behmux2_arch of behmux2 is
begin
    with s select
        f <= x when '0',
            y when '1',
            '0' when others;
end behmux2_arch;
```


- Behavior of 2-1 MUX is written using “with-select-when” statement in VHDL.
  
# Example 2: Synthesis and Simulation

- Synopsys Synthesis
  - Schematics before and after compilation:



- Wave graph simulation:

 




---

# **Structural Modeling**
 
# Structural Description

---

- **Structural** design forces the tool to use certain gates with specified connections for synthesis.
- Gate level structure should be known. Example:



- Components and port mapping is used.
- Structure of the circuit would not alter after synthesis.

# Structural Modeling

---

- The implementation of an entity is done through a set of interconnected components
- Contains:
  - Signal declaration
  - Component instances
  - Port maps
  - May contain wait statements (for simulation)
- Before instantiating the component it should be declared using component declaration.
- Component declaration declares the name of the entity and interface of a component.
- By structural modeling, we can force synthesizer to synthesize an exact gate-level structure with no optimization.

# Example 3: Structural 2-1 Mux

- VHDL Code:

--Example 3: Structural 2-1 Mux

LIBRARY IEEE;

USE IEEE.std\_logic\_1164.all;

USE IEEE.std\_logic\_components.all;

entity and2 is

port ( A, B : in std\_logic;

Z : out std\_logic);

end and2;

architecture beh\_and2 of and2 is

begin -- beh\_and2

Z <= A and B;

end beh\_and2;

LIBRARY IEEE;

USE IEEE.std\_logic\_1164.all;

USE IEEE.std\_logic\_components.all;

entity or2 is

port ( A, B : in std\_logic;

Z : out std\_logic);

end or2;

architecture beh\_or2 of or2 is

begin -- beh\_or2

Z <= A or B;

end beh\_or2;

LIBRARY IEEE;

USE IEEE.std\_logic\_1164.all;

USE IEEE.std\_logic\_components.all;

entity not1 is

port ( A : in std\_logic;

Z : out std\_logic);

end not1;

architecture beh\_not1 of not1 is

begin -- beh\_not1

Z <= not A;

end beh\_not1;

--TOP LEVEL MODULE

LIBRARY IEEE;

USE IEEE.std\_logic\_1164.all;

USE IEEE.std\_logic\_components.all;

ENTITY strucmux2 IS

PORT ( x, y, s : IN std\_logic ;  
f : OUT std\_logic ) ;

END strucmux2;

ARCHITECTURE strucmux2\_arch OF

strucmux2 IS

component and2

port ( A, B : in std\_logic;

Z : out std\_logic);

end component;

component or2

port ( A, B : in std\_logic;

Z : out std\_logic);

end component;

component not1

port ( A : in std\_logic;

Z : out std\_logic);

end component;

SIGNAL tmp1, tmp2, sbar: std\_logic;

BEGIN

S\_1 : not1 port map( A => s, Z =>  
sbar);

S\_2 : and2 port map( A => x, B =>  
sbar, Z => tmp1);


S\_3 : and2 port map( A => y, B => s,  
Z => tmp2);

S\_4 : or2 port map( A => tmp1, B =>  
tmp2, Z => f);

END;
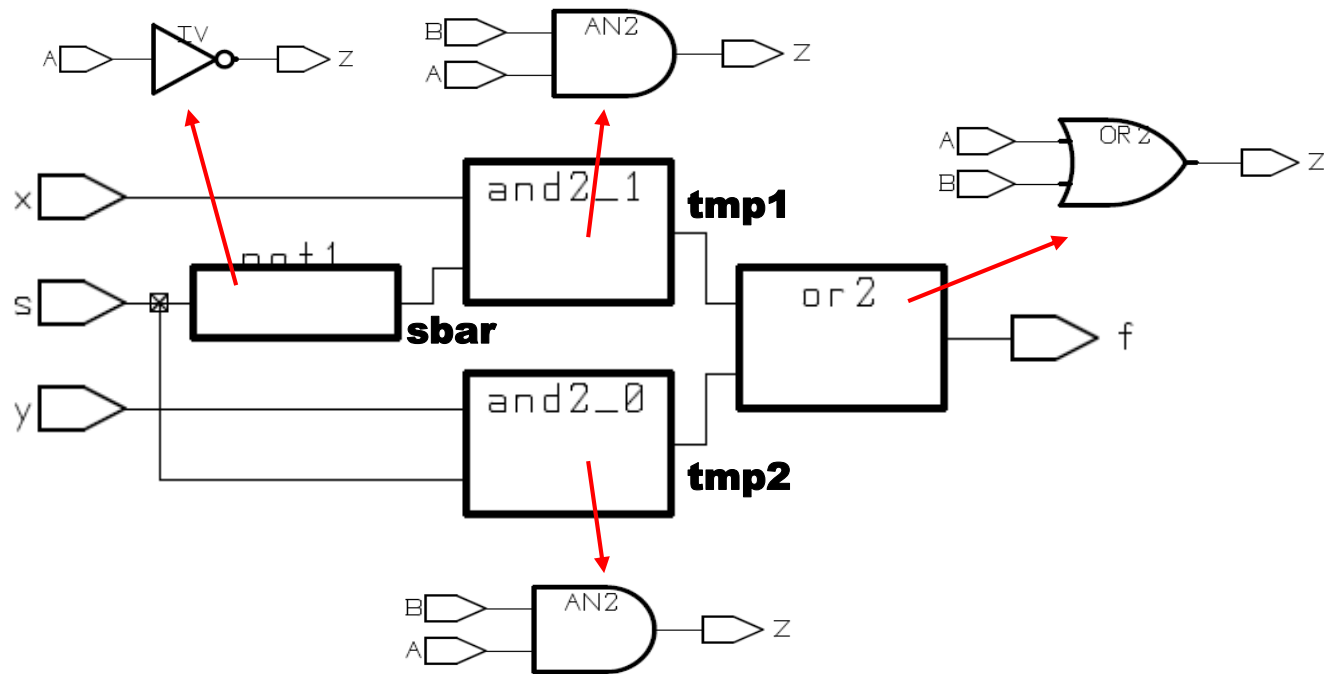
## Example 3: Synthesis

- Schematics after synthesis and compilation:



- Gate level-structure after synthesis remains just as we specified
  - Useful for test (DFT) purposes for specified circuits.

---

# **Don't-Cares in VHDL**

# Don't-Cares in VHDL

---

- In logic synthesis and logic simulation, a *don't-care* is one of the values in a multi-valued logic system that denotes an unknown value, or a value that the designer (for whatever reason) does not care about.
- A don't-care or X value does not exist in hardware. In simulation, an X value can result from two or more sources driving a signal simultaneously, or the stable output of a flip-flop not having been reached.
- In synthesized hardware, however, the actual value of such a signal will be either 0 or 1, but will not be determinable from the circuit's inputs.
- Synthesis tools can use don't-care values to determine where and how to perform area optimization. For example, a synthesis tool can use don't-care values to reduce the number of states and circuit size of finite state machines.

## Example 4: Don't-Cares in VHDL

- Don't-care in digital design denotes a value could be either 0 or 1.
- Don't-cares are specified with '-' in VHDL.
- Suppose  $f$  is a function of minterms of  $a, b, c$ , and  $d$  such that:

$$f(a,b,c,d) = \sum m(1,4,5,7,13) + d(3,6)$$

- Example 4 VHDL Code:

```
--Example 4: VHDL code including don't-cares
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
entity func is
port (
    a,b,c,d: in std_logic;
    f: out std_logic);
end func;
architecture archf of func is
    signal q:std_logic_vector(3 downto 0);
begin
```


```
    q <= a & b & c & d; --concatenating to produce abcd
    with q select
        f<='1' when "0001" | "0100" | "0101" | "0111" | "1101",
        '-' when "0011" | "0110",
        '0' when others;
end archf;
```



 
## Example 4: Synthesis

---

- $f$  is a function of  $a$ ,  $b$ ,  $c$ , and  $d$ :



 - After synthesis and design optimization:



# Don't-Cares in VHDL


---

- When **CASE** or **IF** statements do not cover all possible input conditions *unwanted latches* may be generated to hold the output.
  - Conditions that are not covered do not mean that they are don't-cares!
- Including the final **ELSE** clause or **WHEN OTHERS** clause in an **IF** or **CASE** statement can prevent this unwanted latch from being generated.

# Don't-Cares in VHDL (cont'd)

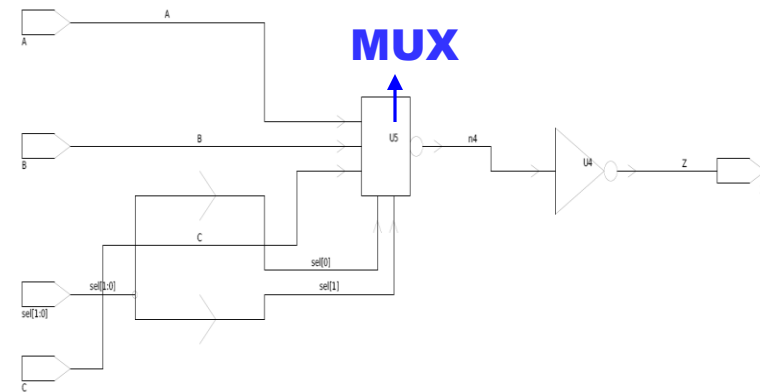- Example 4.1: 3-1 MUX with all conditions covered in **case-when** statement using **when-others**:

```
--Example 4.1: 3-1 MUX with all conditions covered
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
USE IEEE.std_logic_components.all;
entity mux3r is
port ( A, B, C: in std_logic;
      sel: in std_logic_vector(1 downto 0);
      Z : out std_logic);
end mux3r;
ARCHITECTURE mux3r_arch OF mux3r IS
BEGIN
  pMux : process (A,B,C,sel)
  begin
    case sel is
      when "00" => Z <= A;
      when "01" => Z <= B;
      when others => Z <= C;
    end case;
  end process pMux;
END;
```




**No Latch generated in Synthesis**

# Don't-Cares in VHDL (cont'd)

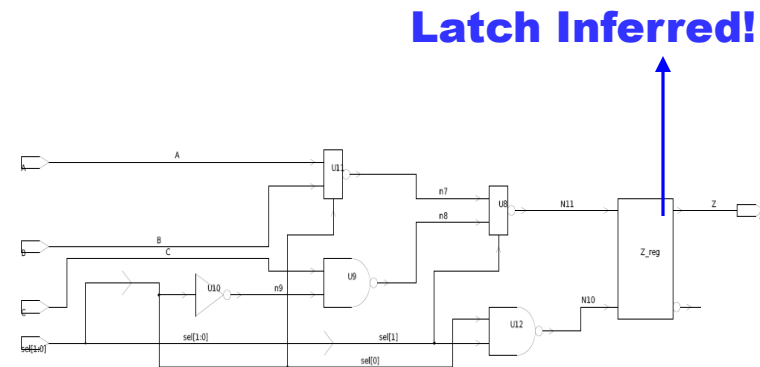- Example 4.2: 3-1 MUX when all conditions are not covered in **case-when** statement:

```
--Example 4.2: 3-1MUX when all conditions are not covered
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
USE IEEE.std_logic_components.all;
entity mux3w is
port ( A, B, C: in std_logic;
      sel: in std_logic_vector(1 downto 0);
      Z : out std_logic);
end mux3w;
ARCHITECTURE mux3w_arch OF mux3w IS
BEGIN
pMux : process (A,B,C,sel)
begin
  case sel is
    when "00" => Z <= A;
    when "01" => Z <= B;
    when "10" => Z <= C;
    when others => NULL;
  end case;
end process pMux;
END;
```



---

# **Synthesizer Analysis Report**

# Metrics Often Reported

---

- The three main metrics of the synthesized design (and other metrics) can be reported by the tool.
- Depending on which library Synopsys tool uses (**class**, **gtech**, etc.), design metric values would differ.
- Total combinational **area** is reported in terms of equivalent 2-input NAND gates
- Non-combinational area would be non-zero for sequential designs containing flip-flops.
- Total dynamic **power** can be reported by the tool.
- **Timing** characteristics can be reported, and the values are given with respect to rising (**r**) and falling (**f**) times in nanoseconds.

# Area Report (2-Input MUX Example)

---

\*\*\*\*\*

Report : area

Design : behmux2

Version: V-2003.12

Date : Sun Jan 11 03:36:57 2009

\*\*\*\*\*

Library(s) Used:

class (File: /home/cad/synopsys-2003/syn/libraries/syn/class.db)

Number of ports: 4

Number of nets: 5

Number of cells: 2

Number of references: 2

Combinational area: 4.000000

Noncombinational area: 0.000000

Net Interconnect area: undefined (Wire load has zero net area)

Total cell area: 4.000000

Total area: undefined

1

design\_analyzer>

\*\*\*\*\*

# Power Report

\*\*\*\*\*

Report : power

-analysis\_effort low

Design : behmux2

Version: V-2003.12

Date : Sun Jan 11 03:36:57 2009

\*\*\*\*\*

Library(s) Used:

class (File: /home/cad/synopsys-2003/syn/libraries/syn/class.db)

Warning: The library cells used by your design are not characterized for internal power. (PWR-26)

Operating Conditions:

Wire Load Model Mode: top

Design	Wire Load Model	Library
--------	-----------------	---------

-----

behmux2	05x05	class
---------	-------	-------

Global Operating Voltage = 5

Power-specific unit information :

Voltage Units = 1V

Capacitance Units = 0.100000ff

Time Units = 1ns

Dynamic Power Units = 100nW (derived from V,C,T units)

Leakage Power Units = Unitless

Cell Internal Power = 0.0000 nW (0%)

Net Switching Power = 4.5201 uW (100%)

-----

Total Dynamic Power = 4.5201 uW (100%)

Cell Leakage Power = 0.0000

design\_analyzer>

\*\*\*\*\*



# Timing Report

Report : timing

-path full  
-delay max  
-max\_paths 1

Design : behmux2

Version: V-2003.12

Date : Sun Jan 11 03:36:57 2009

\*\*\*\*\*

Operating Conditions:

Wire Load Model Mode: top

Startpoint: x (input port)

Endpoint: f (output port)

Path Group: (none)

Path Type: max

Des/Clust/Port	Wire Load Model	Library
----------------	-----------------	---------

behmux2	05x05	class
---------	-------	-------

Point	Incr	Path
-------	------	------

input external delay	0.00	0.00 f
----------------------	------	--------

x (in)	0.00	0.00 f
--------	------	--------

U13/Z (IV)	0.58	0.58 r
------------	------	--------

U12/Z (EON1)	0.90	1.48 f
--------------	------	--------

f (out)	0.00	1.48 f
---------	------	--------

data arrival time		1.48
-------------------	--	------

(Path is unconstrained)

design\_analyzer>

# Report (cont'd)

---

- Report of Area, Power and Timing:

```
(Path is unconstrained)
1
design_analyzer>
*****
Report : area
Design : behmux2
Version: V-2003.12
Date   : Sun Jan 11 03:37:01 2009
*****
Library(s) Used:
    class (File: /home/cad/synopsys-2003/syn/libraries/syn/class.db)
Number of ports:          4
Number of nets:           5
Number of cells:          2
Number of references:      2
Combinational area:       4.000000
Noncombinational area:    0.000000
Net Interconnect area:    undefined (Wire load has zero net area)
Total cell area:          4.000000
Total area:               undefined
1
design_analyzer>
*****
```

# Report (cont'd)

- Report of Area, Power and Timing:

Report : power

-analysis\_effort low

Design : behmux2

Version: V-2003.12

Date : Sun Jan 11 03:37:01 2009

\*\*\*\*\*

Library(s) Used:

class (File: /home/cad/synopsys-2003/syn/libraries/syn/class.db)

Warning: The library cells used by your design are not characterized for internal power. (PWR-26)

Operating Conditions:

Wire Load Model Mode: top

Design	Wire Load Model	Library
behmux2	05x05	class

Global Operating Voltage = 5

Power-specific unit information :

Voltage Units = 1V

Capacitance Units = 0.100000ff

Time Units = 1ns

Dynamic Power Units = 100nW (derived from V,C,T units)

Leakage Power Units = Unitless

Cell Internal Power = 0.0000 nW (0%)

Net Switching Power = 4.5201 uW (100%)

-----  
Total Dynamic Power = 4.5201 uW (100%)

# Report (cont'd)

- Report of Area, Power and Timing:

```
Cell Leakage Power      =    0.0000
1
design_analyzer>
*****
Report : timing
      -path full
      -delay max
      -max_paths 1
```

```
Design : behmux2
Version: V-2003.12
Date   : Sun Jan 11 03:37:01 2009
```

```
*****
```

Operating Conditions:

```
Wire Load Model Mode: top
  Startpoint: x (input port)
  Endpoint: f (output port)
  Path Group: (none)
  Path Type: max
```

Des/Clust/Port	Wire Load Model	Library
----------------	-----------------	---------

behmux2	05x05	class
---------	-------	-------

Point	Incr	Path
-------	------	------

```
input external delay
      0.00      0.00 f
x (in)
      0.00      0.00 f
U13/Z (IV)
      0.58      0.58 r
U12/Z (EON1)
      0.90      1.48 f
f (out)
      0.00      1.48 f
data arrival time
      1.48
```

-----  
-----  
(Path is unconstrained)

```
1
design_analyzer>
```

---

# **Parametric Coding in VHDL**

# Parametric Coding in VHDL

---


- The concept of *generics* is often used to parameterize components.
- Example 5.1: 32-bit 2-input MUX:

```
--Example 5.1: 32-bit input MUX
library IEEE;
use IEEE.std_logic_1164.all;
entity mux32 is
  generic(n : natural := 31);
port(
  x : in std_logic_vector (n downto 0);
  y : in std_logic_vector (n downto 0);
  s : in std_logic;
  f : out std_logic_vector (n downto 0));
end entity mux32;
architecture behavior of mux32 is
begin -- behavior -- no process needed with concurrent statements
  f <= y when s='1' or s='H' else x;
end architecture behavior; -- of mux32
```
 
## Example 5.1 (cont'd)

---

- Schematics after synthesis and design optimization:
- The **generic** statement allows parametric settings so that the design could be compiled for desired values.



# Parametric Loop in VHDL


- Generic statement required in entity.
- Loop is declared using **for-loop** statement
- Example 5.2: VHDL code for a 32-bit adder:

```
-- Example 5.2: 32-bit input adder
library IEEE;
use IEEE.std_logic_1164.all;
entity add32 is
    generic(n : natural := 31);
    port (a      : in  std_logic_vector (n downto 0);
          b      : in  std_logic_vector (n downto 0);
          cin    : in  std_logic;
          sum    : out std_logic_vector (n downto 0);
          cout   : out std_logic);
end entity add32;
architecture behavior of add32 is
begin -- behavior
    adder: process
        variable carry : std_logic; -- internal
        variable isum  : std_logic_vector(n downto 0); -- internal
    begin
        carry := cin;
        for i in 0 to n loop
            isum(i) := a(i) xor b(i) xor carry;
            carry := (a(i) and b(i)) or (a(i) and carry) or (b(i) and carry);
        end loop;
        sum <= isum;
        cout <= carry;
    end process adder;
end architecture behavior; -- of add32
```


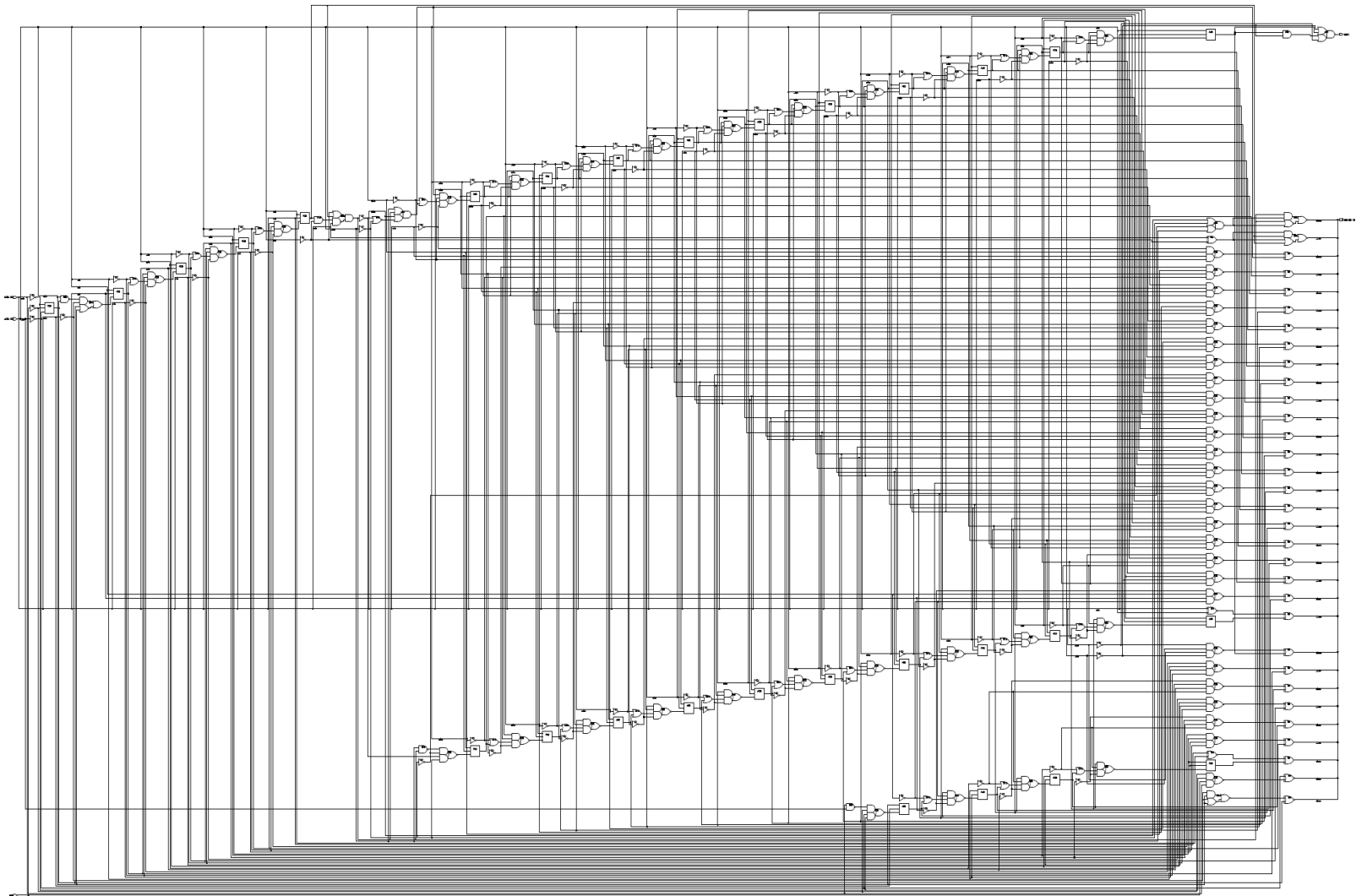
## Example 5.2 (cont'd)

- Schematic after synthesis and design optimization:




# Parametric Coding in VHDL (cont'd)

- Iterative commands declared using **for-generate** statements
  - Makes copies of concurrent statements
- Example 5.3: 32-bit 2-input MUX with for-generate:

```
--Example 5.3: 32-bit input MUX with for-generate statements
library IEEE;
use IEEE.std_logic_1164.all;
entity mux32_it is
  generic(n : natural := 31);
port(
  x : in std_logic_vector (n downto 0);
  y : in std_logic_vector (n downto 0);
  s : in std_logic;
  f : out std_logic_vector (n downto 0));
end entity mux32_it;
architecture mux32_it_arch of mux32_it is
begin
  gen1: for i in 0 to n generate
    f(i) <= (x(i) and not s) or (s and y(i));
  end generate gen1;
end architecture mux32_it_arch;
```
 
## Example 5.3 (cont'd)

- The **generate** statement combines concurrent statements with a looping capability
- Schematics after synthesis and design optimization ->
- The same gate level structure achieved as in Example 5.1




---

# **Hierarchical Design in VHDL**
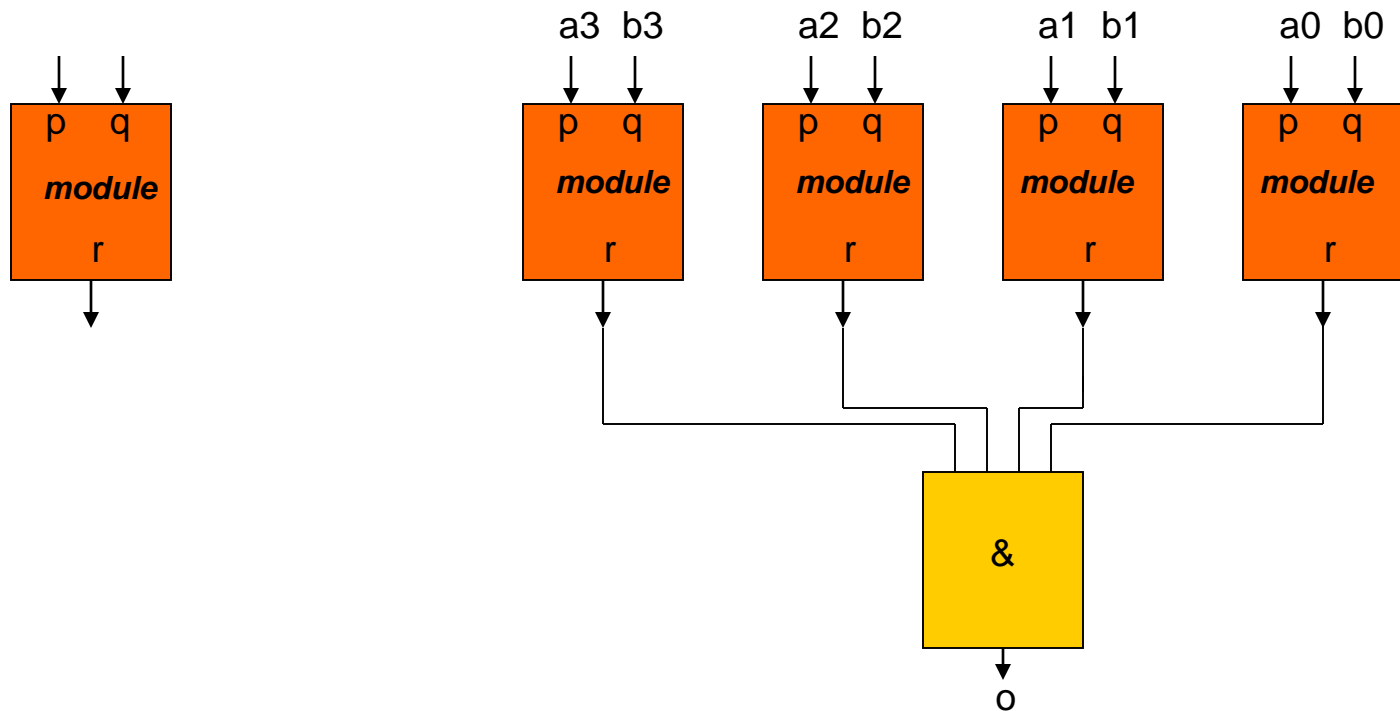
# Hierarchical Design in VHDL

- VHDL supports design by creating modules of circuit components that can be used in another design
- Components and port mapping used in top level design




# Example 6: A hierarchical Design

```
--Example 6: A hierarchical design
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
USE IEEE.std_logic_components.all;
entity module is
port ( A, B : in std_logic;
      Z : out std_logic);
end module;
architecture module_arch of module is
begin
    Z <= (A and not B) or (not A and B);
end module_arch;


-----

--TOP LEVEL MODULE
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
USE IEEE.std_logic_components.all;
ENTITY hier IS
PORT ( a0, b0, a1, b1, a2, b2, a3, b3: IN    std_logic;
      o : OUT    std_logic ) ;
END hier;
ARCHITECTURE hier_arch OF hier IS
component module
port ( A, B : in std_logic;
      Z : out std_logic);
end component;
SIGNAL p, q, r, s: std_logic;
BEGIN
M_1 : module port map( A => a0, B => b0, Z => p);
M_2 : module port map( A => a1, B => b1, Z => q);
M_3 : module port map( A => a2, B => b2, Z => r);
M_4 : module port map( A => a3, B => b3, Z => s);
o <= p and q and r and s;
END;
```

 
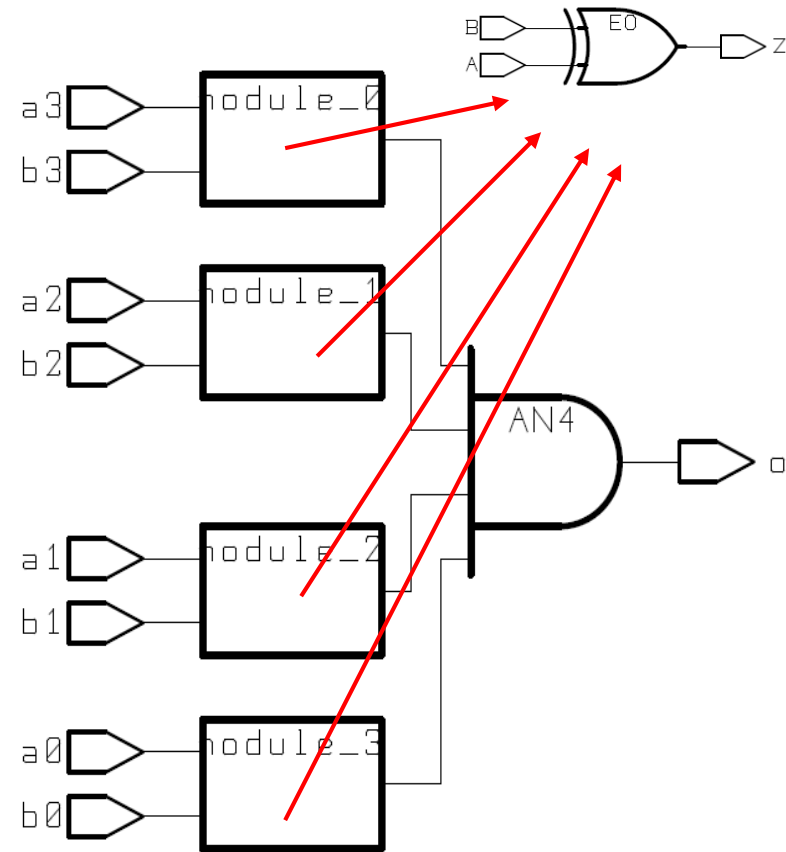
## Example 6: Synthesis

- Schematics design after Synopsys synthesis, design optimization and compilation:
- The module in this design is an **XOR** gate
- Each module would be optimized alone
- Does not necessarily optimize the whole design altogether



---

# **Sequential Modeling**




# Modeling Flip-Flops

- D-flip-flop behavior

 -Example 7.1: D-flip-flop with reset

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
entity dff is
port( d:in std_logic;
      clk,rst:in std_logic;
      q:out std_logic);
end dff;
architecture dff_arch of dff is
begin
  process(rst, clk)
  begin
    if rst = '1' then
      q <= '0';
    elsif clk'event and clk = '1' then
      q <= d; --rising edge triggered
    end if;
  end process;
end dff_arch;
```



# Negative Edge Triggered D-Flip-flop

- VHDL Code:


```
-- Example 7.2 Negative Edged Triggered DFF
library ieee;
use ieee.std_logic_1164.all;
```

```
entity dflipn is port (
    d,clk: in std_logic;
    q: out std_logic );
end dflipn;
```

```
architecture dflipn_arch of dflipn is
begin
```

```
    process(clk)
    begin
        if (clk'event and clk = '0') then
            q <= d; -- set the changes to the negative edge of clock
        end if;
    end process;
```

```
end dflipn_arch;
```

 

---

# **Importance of Sensitivity List**

# Process and Sensitivity List

---

- A process is a wrapper for sequential statements.
  - Sequential statements model combinational or synchronous logic (or both).
  - Statements within a process are executed sequentially.
  - Beware! Signal assignments are BOTH concurrent and sequential.
- A process is concurrent with other concurrent statements in an architecture.
- An architecture can have multiple processes.
- Signal changes in the sensitivity list cause the process to "run" or be evaluated.
  - All sequential statements in the process are "executed".
  - Variables are updated as statements are sequentially "executed".
  - Signal updates are scheduled as statements are sequentially "executed".
  - Signal updates occur when the process is suspended (finished).
- A common error is to think that signal updates take place when a sequential statement is executed.

# Importance of Sensitivity List

---

- The signal sensitivity list is used to specify which signals should cause the process to be re-evaluated.
- Whenever any event occurs on one of the signals in the sensitivity list, the process is re-evaluated.
- A process is evaluated by performing each statement that it contains. These statements (the body of the process) appear between the **begin** and **end** keywords.
- Synthesis programs do not care about sensitivity list but gives you a warning if they are not complete.

## Example 8: Importance of Sensitivity List

- If “d” input is added to the sensitivity list of D-Flip-Flop (Example 7.1), there would just be an overhead for simulation, but no false behavior for simulation or synthesis would be observed if it is not on the list.
  - This behavior is because of the rising-edge detection of D-Flip-Flop.
- Transparent latch should have the “d” input added to the sensitivity list, as change in input should be reflected at output when “en” is high.
- VHDL Code for Latch with input “d” on sensitivity list:

```
--Example 8.1: Transparent Latch
library ieee;
use ieee.std_logic_1164.all;
entity mylatch is
port( d:in std_logic;
      en:in std_logic;
      o:out std_logic);
end mylatch;
```

```
architecture mylatch_arch of mylatch is
begin
```

```
Latch_Data:process(en,d)
--sensitivity list
begin
    if (en = '1') then
        o <= d;
    -- If en = 0, then o keeps its old value.
    end if;
end process Latch_Data;
end mylatch_arch;
```

## Example 8 (cont'd)

---


- For combinational logic or latches you have to take more care with the sensitivity list.
- If “d” input is not on sensitivity list of the latch, -> **wrong functionality in simulation.**
- VHDL code of a latch with incorrect behavior:

```
--Example 8.2: Latch with incorrect behavior
library ieee;
use ieee.std_logic_1164.all;
entity mylatch is
port( d:in std_logic;
      en:in std_logic;
      o:out std_logic);
end mylatch;
```

```
architecture mylatch_arch of mylatch is
begin
  Latch_Data: process(en)
--sensitivity list
  begin
    if (en ='1') then
      o <= d;
    -- If en = 0, then o keeps its old value.
    end if;
  end process Latch_Data;
end mylatch_arch;
```
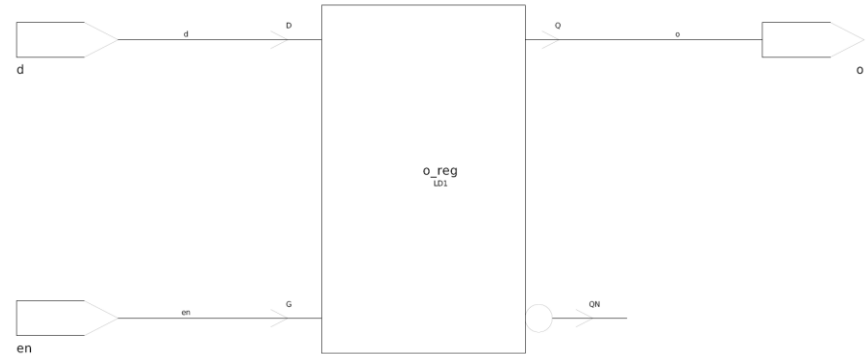
# Example 8: Synthesis & Test bench

- Synthesis of both example 8.1 and 8.2 codes look alike!



- VHDL Code for Test bench:

```
--Test bench for Example 8: Latch
library IEEE;
USE IEEE.std_logic_1164.all;
entity tbmylatch is
end tbmylatch;
architecture tbmylatch_arch of tbmylatch is
  component mylatch
    port( d:in std_logic;
          en:in std_logic;
          o:out std_logic);
  end component;
end tbmylatch;
```

```
signal in_d, in_en, out_o: std_logic := '0';
begin
  imylatch:mylatch port map(d=>in_d, en=>in_en, o=>out_o);
  in_en<= not in_en after 10 ns;
  in_d<='0','1' after 25 ns, '0' after 35 ns;
end tbmylatch_arch;


configuration cf_mylatch of tbmylatch is
  for tbmylatch_arch
    for imylatch:mylatch
      use entity WORK.mylatch (mylatch_arch);
    end for;
  end for;
end cf_mylatch;
```




## Example 8: Simulation

- Simulation results of Example 8.1:

**Correct**

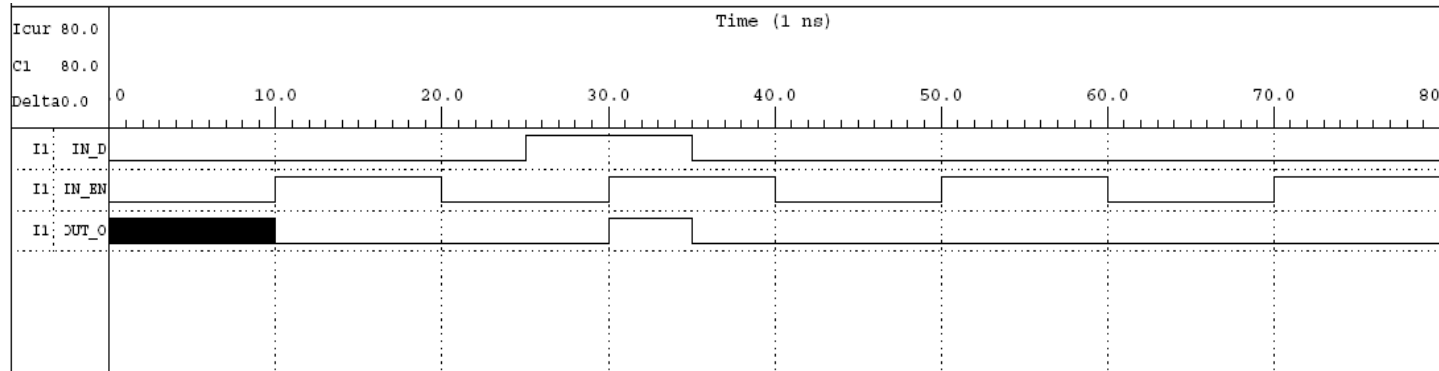

- Simulation results of Example 8.2:

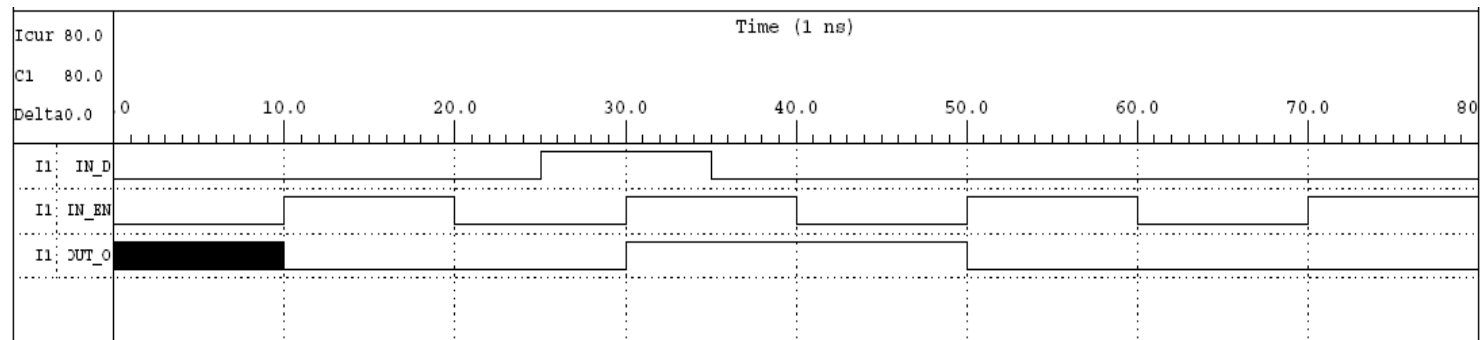

**Incorrect functionality**

---

# **Modeling Sequential FSM**


# Sequential Logic Using VHDL

---

- Finite State Machine (**FSM**)
  - A circuit that has defined states and can switch between them if certain conditions exist
- Moore Machine
  - A **Moore** machine has output(s) that depend on state only
  - The FSM has the output(s) written in the state itself
- Mealy Machine
  - A **Mealy** machine has output(s) that depend on both the state and input(s)
  - The FSM has the output written on edges

# Moore Machine

State Diagram:

 

Transition Table:

Present State	Next State		Output (Z)
	x = 0	x = 1	
S0	S0	S2	0
S1	S0	S2	1
S2	S2	S3	1
S3	S3	S1	0

# Example 9: Moore Machine

- VHDL Code:

```
--Example 9: Moore machine
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity moore is
port( x, clk:in bit;
      Z:out bit);
end moore;

architecture moore_arch of moore is
type state_type is (S0, S1, S2, S3);
signal current_state, next_state: state_type;


begin
  --process to hold synchronous elements (flip-flops)
  SYNCH:process
  begin
    wait until clk'event and clk='1';
    current_state <= next_state;
  end process;
```

```
--process to hold combinational logic
COMBIN:process (current_state, x)
begin
  case current_state is
    when S0 =>
      Z <= '0';
      if x='0' then
        next_state <= S0;
      else
        next_state <= S2;
      end if;
    when S1 =>
      Z <= '1';
      if x='0' then
        next_state <= S0;
      else
        next_state <= S2;
      end if;
    when S2 =>
      Z <= '1';
      if x='0' then
        next_state <= S2;
      else
        next_state <= S3;
      end if;
    when S3 =>
      Z <= '0';
      if x='0' then
        next_state <= S3;
      else
        next_state <= S1;
      end if;
  end case;
end process;
end moore_arch;
```

Output is defined outside if-then-else statement


## Example 9: Moore Machine (cont'd)

- Schematics of Synthesized logic:

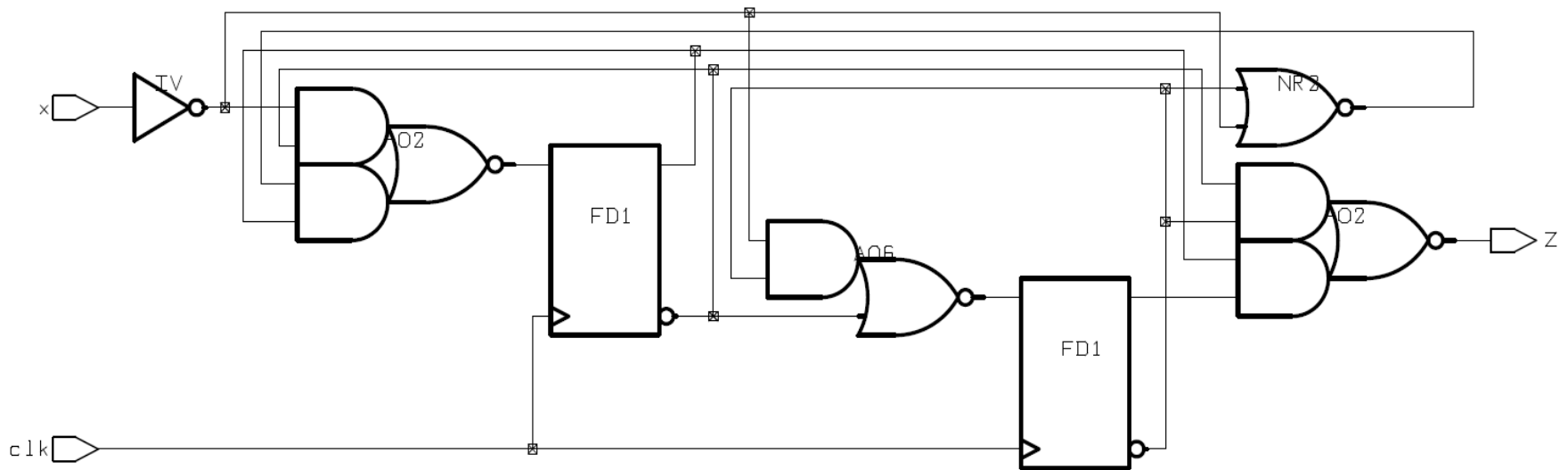

# Mealy Machine

State Diagram:

 

Transition table:

Present State	Next State		Output (Z)	
	x = 0	x = 1	x = 0	x = 1
S0	S0	S2	0	1
S1	S0	S2	0	0
S2	S2	S3	1	0
S3	S3	S1	0	1

# Example 10: Mealy Machine

- VHDL Code:

```
--Example 10: Mealy machine
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity mealy is
port( x, clk:in bit;
      Z:out bit);
end mealy;

architecture mealy_arch of mealy is
type state_type is (S0, S1, S2, S3);
signal current_state, next_state: state_type;

begin
  --process to hold synchronous elements (flip-flops)
  SYNCH:process
  begin
    wait until clk'event and clk='1';
    current_state <= next_state;
  end process;
```

```
--process to hold combinational logic
COMBIN:process (current_state, x)
begin
```

```
  case current_state is
```

```
    when S0 =>
      if x='0' then
        Z <= '0';
        next_state <= S0;
      else
        Z <= '1';
        next_state <= S2;
      end if;
```

```
    when S1 =>
      if x='0' then
        Z <= '0';
        next_state <= S0;
      else
        Z <= '0';
        next_state <= S2;
      end if;
```

```
    when S2 =>
      if x='0' then
        Z <= '1';
        next_state <= S2;
      else
        Z <= '0';
        next_state <= S3;
      end if;
```


```
    when S3 =>
      if x='0' then
        Z <= '0';
        next_state <= S3;
      else
        Z <= '1';
        next_state <= S1;
      end if;
```

```
  end case;
end process;
end mealy_arch;
```

**Output is defined  
inside if-then-else  
statement**



\_\_\_\_\_

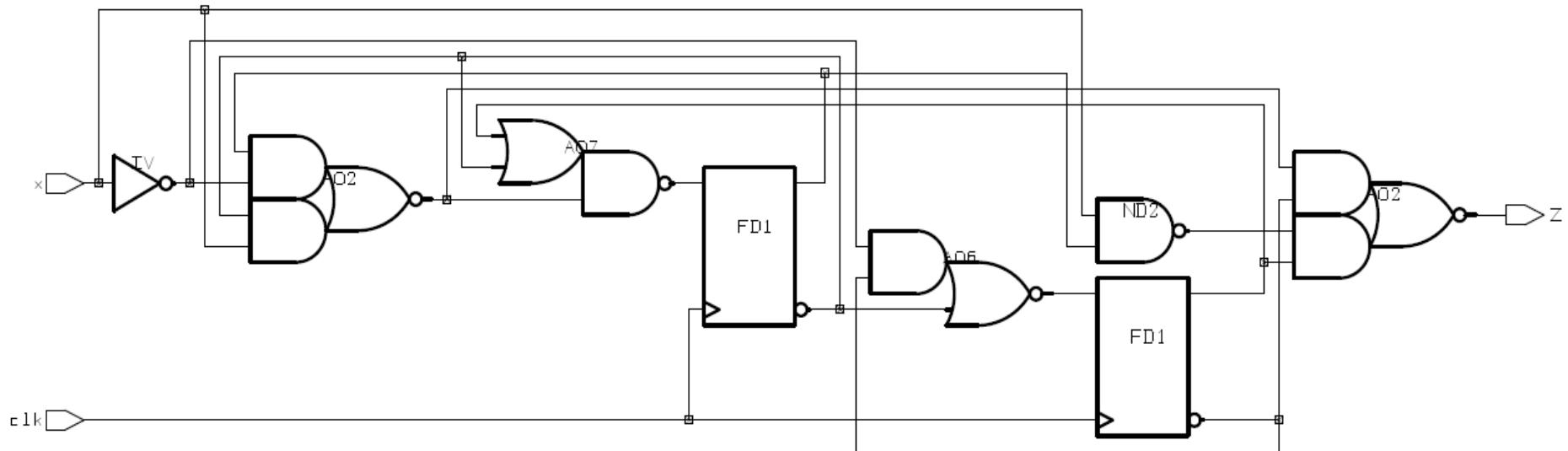

---

# **Asynchronous Modeling**

# Asynchronous Design

---

- An asynchronous circuit is one in which synchronization is performed without a global clock
- Advantages:
  - Elimination of clock skew problems.
  - Average-case performance.
  - Adaptivity to processing and environmental variations.
  - Component modularity and reuse.
  - Lower system power requirements.
  - Reduced noise.

# Example 11: Asynchronous Design

- Example 11: Design an asynchronous sequential circuit with two inputs P (pulse) and R (reset), and a single output Z that is normally 0. The output should be set to 1 whenever a  $0 \rightarrow 1$ , or  $1 \rightarrow 0$  transition occurs on P, and should be reset to 0 whenever R is 1

— Flow Table (non-optimized)

Meaning		PR				Z
		00	01	11	10	
Idle, p=0	S0	<b>S0</b>	S3	—	S1	0
Rising, no reset	S1	S2	—	S4	<b>S1</b>	1
Falling, no reset	S2	<b>S2</b>	S3	—	S1	1
Reset when p=0	S3	S0	<b>S3</b>	S4	—	0
Reset when p=1	S4	—	S3	<b>S4</b>	S5	0
Idle, p=1	S5	S2	—	S4	<b>S5</b>	0

# Example 11: VHDL Code

```
--Example 11: Asynchronous modeling in VHDL
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
entity asyn is
port (
    p,r: in std_logic;
    z: out std_logic);
end asyn;
architecture asyn_arch of asyn is
    type states is (s0, s1, s2, s3, s4, s5);


    signal currentstate : states:= s0;
begin
    state_trans: process(p,r)
    begin
        case currentstate is
            when s0=>
                if (p='0') and (r='0') then
                    currentstate<=s0;
                    z<='0';
                elsif (p='0') and (r='1') then
                    currentstate<=s3;
                    z<='0';
                elsif (p='1') and (r='1') then
                    currentstate<=s4;
                    z<='0';
                else
                    currentstate<=s1;
                    z<='1';
                end if;
            when s1=>
                if (p='0') and (r='0') then
                    currentstate<=s2;
                    z<='1';
                elsif (p='0') and (r='1') then
                    currentstate<=s3;
                    z<='0';
                elsif (p='1') and (r='1') then
                    currentstate<=s4;
                    z<='0';
                else
                    currentstate<=s1;
                    z<='1';
                end if;
            when s2=>
                if (p='0') and (r='0') then
                    currentstate<=s2;
                    z<='1';
                elsif (p='0') and (r='1') then
                    currentstate<=s3;
                    z<='0';
                elsif (p='1') and (r='1') then
                    currentstate<=s4;
                    z<='0';
                else
                    currentstate<=s1;
                    z<='1';
                end if;
            when s3=>
                if (p='0') and (r='0') then
                    currentstate<=s0;
                    z<='0';
                elsif (p='0') and (r='1') then
                    currentstate<=s3;
                    z<='0';
                elsif (p='1') and (r='1') then
                    currentstate<=s4;
                    z<='0';
                else
                    currentstate<=s1;
                    z<='1';
                end if;
            when s4=>
                if (p='0') and (r='0') then
                    currentstate<=s2;
                    z<='1';
                elsif (p='0') and (r='1') then
                    currentstate<=s3;
                    z<='0';
                elsif (p='1') and (r='1') then
                    currentstate<=s4;
                    z<='0';
                else
                    currentstate<=s1;
                    z<='1';
                end if;
            when s5=>
                if (p='0') and (r='0') then
                    currentstate<=s2;
                    z<='1';
                elsif (p='0') and (r='1') then
                    currentstate<=s3;
                    z<='0';
                elsif (p='1') and (r='1') then
                    currentstate<=s4;
                    z<='0';
                else
                    currentstate<=s5;
                    z<='0';
                end if;
        end case;
    end process state_trans;
end asyn_arch;
```

```
when s2=>
    if (p='0') and (r='0') then
        currentstate<=s2;
        z<='1';
    elsif (p='0') and (r='1') then
        currentstate<=s3;
        z<='0';
    elsif (p='1') and (r='1') then
        currentstate<=s4;
        z<='0';
    else
        currentstate<=s1;
        z<='1';
    end if;
when s3=>
    if (p='0') and (r='0') then
        currentstate<=s0;
        z<='0';
    elsif (p='0') and (r='1') then
        currentstate<=s3;
        z<='0';
    elsif (p='1') and (r='1') then
        currentstate<=s4;
        z<='0';
    else
        currentstate<=s1;
        z<='1';
    end if;
when s4=>
    if (p='0') and (r='0') then
        currentstate<=s2;
        z<='1';
    elsif (p='0') and (r='1') then
        currentstate<=s3;
        z<='0';
    elsif (p='1') and (r='1') then
        currentstate<=s4;
        z<='0';
    else
        currentstate<=s1;
        z<='1';
    end if;
```

```
when s5=>
    if (p='0') and (r='0') then
        currentstate<=s2;
        z<='1';
    elsif (p='0') and (r='1') then
        currentstate<=s3;
        z<='0';
    elsif (p='1') and (r='1') then
        currentstate<=s4;
        z<='0';
    else
        currentstate<=s5;
        z<='0';
    end if;
end case;
end process state_trans;
end asyn_arch;
```

# Example 11: Synthesis

- Schematics of logic synthesis:

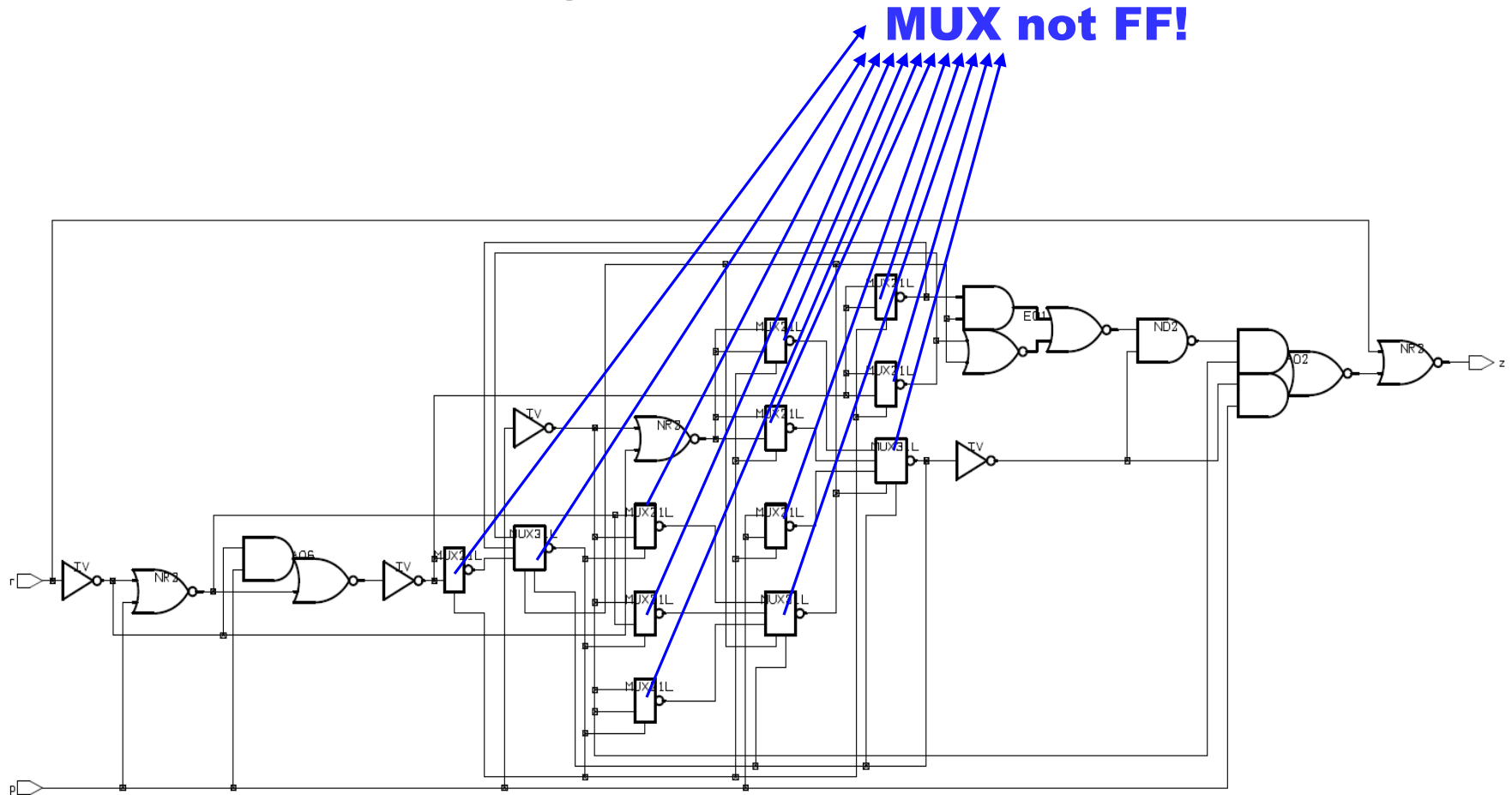

---

# **Parallelism and Interaction Among Units**

# Parallelism and Interaction Among Units

- VHDL concurrent statements allows parallelism among units.


```
--Example 12: Parallelism & Interaction
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
USE IEEE.std_logic_components.all;
```

```
-----
entity myand is
port ( A, B : in std_logic;
      Z : out std_logic);
end myand;
architecture myand_arch of myand is
begin
  Z <= A and B after 10 ns;
end myand_arch;
-----
```

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
USE IEEE.std_logic_components.all;
```

```
entity myxor is
port ( A, B : in std_logic;
      Z : out std_logic);
end myxor;
architecture myxor_arch of myxor is
begin
  Z <= A xor B after 20 ns;
end myxor_arch;
```


```
--TOP LEVEL MODULE
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
USE IEEE.std_logic_components.all;
ENTITY mydesign IS
  PORT ( x, y : IN  std_logic ;
        f, g : OUT  std_logic ) ;
END mydesign;
ARCHITECTURE mydesign_arch OF mydesign IS
  component myand
  port ( A, B : in std_logic;
        Z : out std_logic);
  end component;
  component myxor
  port ( A, B : in std_logic;
        Z : out std_logic);
  end component;
BEGIN
  U_1 : myand port map( A => x, B => y, Z => f);
  U_2 : myxor port map( A => x, B => y, Z => g);
END;
```

 



# Example 12: Synthesis

- Schematic of Synthesis:

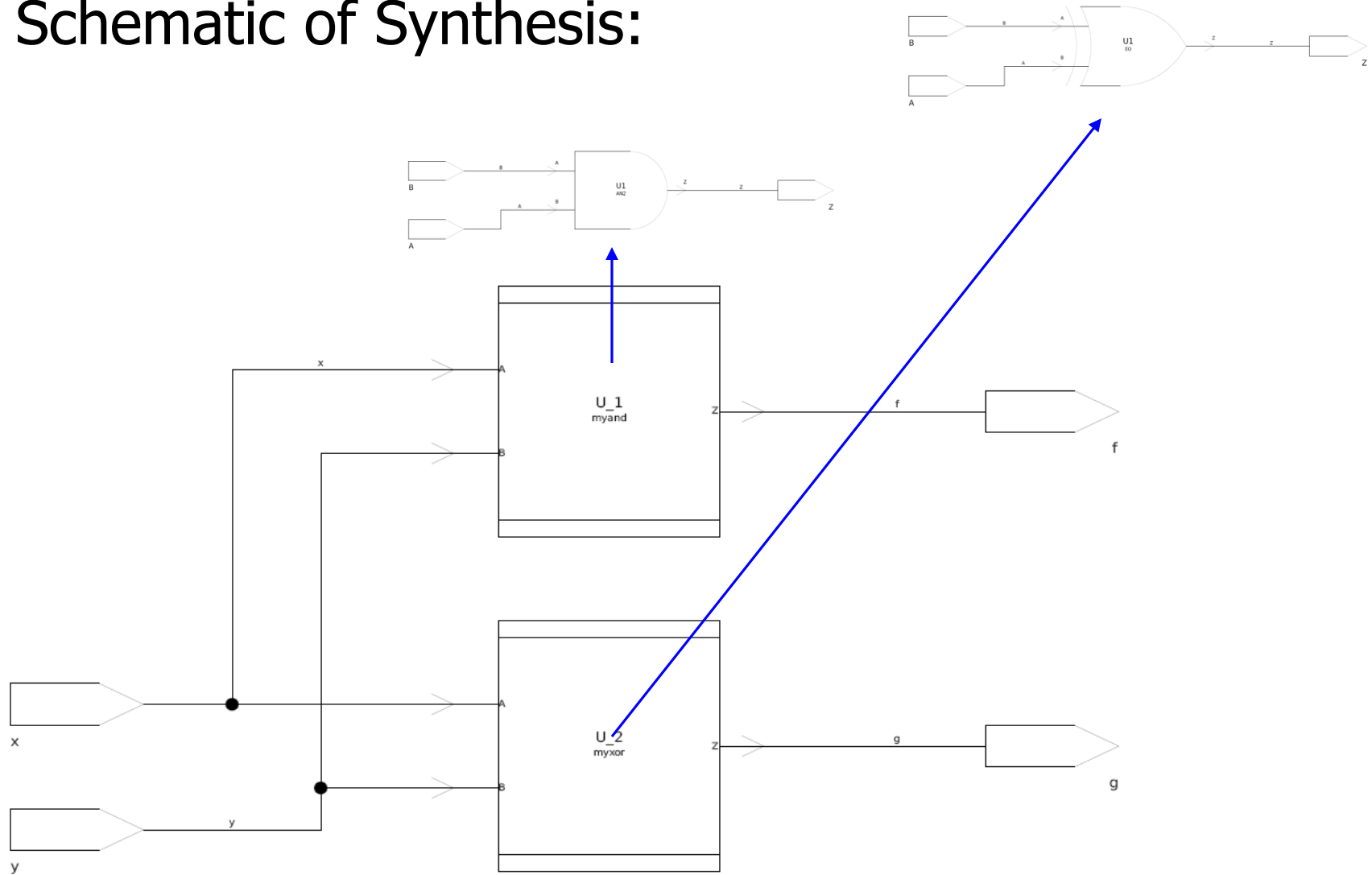


# Example 12: Test Bench

- Test bench:

```
--Test bench for Example 12
library IEEE;
USE IEEE.std_logic_1164.all;
USE IEEE.std_logic_components.all;
entity tbmydesign is
end tbmydesign;
architecture tbmydesign_arch of tbmydesign is
  component myand
    port ( A, B : in std_logic;
          Z : out std_logic);
  end component;
  component myxor
    port ( A, B : in std_logic;
          Z : out std_logic);
  end component;
  component mydesign
    PORT ( x, y :in std_logic;
          f, g :out std_logic);
  end component;
  signal in_x, in_y, out_f, out_g: std_logic;
begin
  imydesign:mydesign port map(x=>in_x, y=>in_y, f=>out_f, g=>out_g);
  in_x<='0';
  in_y<='1';
  end tbmydesign_arch;
configuration cf_mydesign of tbmydesign is
  for tbmydesign_arch
  for imydesign:mydesign
  use entity WORK.mydesign(mydesign_arch);
  end for;
  end for;
end cf_mydesign;
```

# Example 12: Simulation

- Wave graph Simulation:

 

- Outputs observed at respective times

---

# **Implementing Memory in VHDL**

# Example 13: Memory Module in VHDL

```
--Example 12: A 4*4 RAM module
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity SRAM is
generic(
    width:      integer:=4;
    depth:      integer:=4;
    addr:       integer:=2;
port( Clock:   in std_logic;
      Enable:  in std_logic;
      Read:    in std_logic;
      Write:   in std_logic;
      Read_Addr: in std_logic_vector(addr-1 downto 0);
      Write_Addr: in std_logic_vector(addr-1 downto 0);
      Data_in: in std_logic_vector(width-1 downto 0);
      Data_out: out std_logic_vector(width-1 downto 0)
);
end SRAM;

architecture behav of SRAM is

type ram_type is array (0 to depth-1) of
    std_logic_vector(width-1 downto 0);
signal tmp_ram: ram_type;

begin
    -- Read Functional Section
    process(Clock, Read)
    begin
        if (Clock'event and Clock='1') then
            if Enable='1' then
                if Read='1' then
                    -- builtin function conv_integer change the type
                    -- from std_logic_vector to integer
                    Data_out <= tmp_ram(conv_integer(Read_Addr));
                else
                    Data_out <= (Data_out'range => 'Z');
                end if;
            end if;
        end if;
    end process;
```

```
-- Write Functional Section
process(Clock, Write)
begin
    if (Clock'event and Clock='1') then
        if Enable='1' then
            if Write='1' then
                tmp_ram(conv_integer(Write_Addr)) <= Data_in;
            end if;
        end if;
    end process;
end behav;
```

**Write**

**Use of arrays**

**Read**

# Example 13: Synthesis

- Schematics of logic synthesis:

